



Figure 1 Amplifier A_1 amplifies and inverts the common-mode voltage by a factor of -10 . Then, the circuit applies this signal to an array of passive summation networks. An analog multiplexer selects the desired input signal, and op amp A_2 supplies a compensating gain.