



Figure 2 This circuit puts unipolar drive in a PID-feedback loop to stabilize the temperature of the target device.