



Figure 1 This DAC circuit sums two 16-bit PWM signals using precision analog switches to achieve 32-bit resolution.