



Figure 1 This circuit periodically sets the thermoelectric cooler's drive current to zero, sampling the Seebeck voltage and holding it in a storage capacitor to achieve stable temperature control with real-world heat sinks and thermocouples.