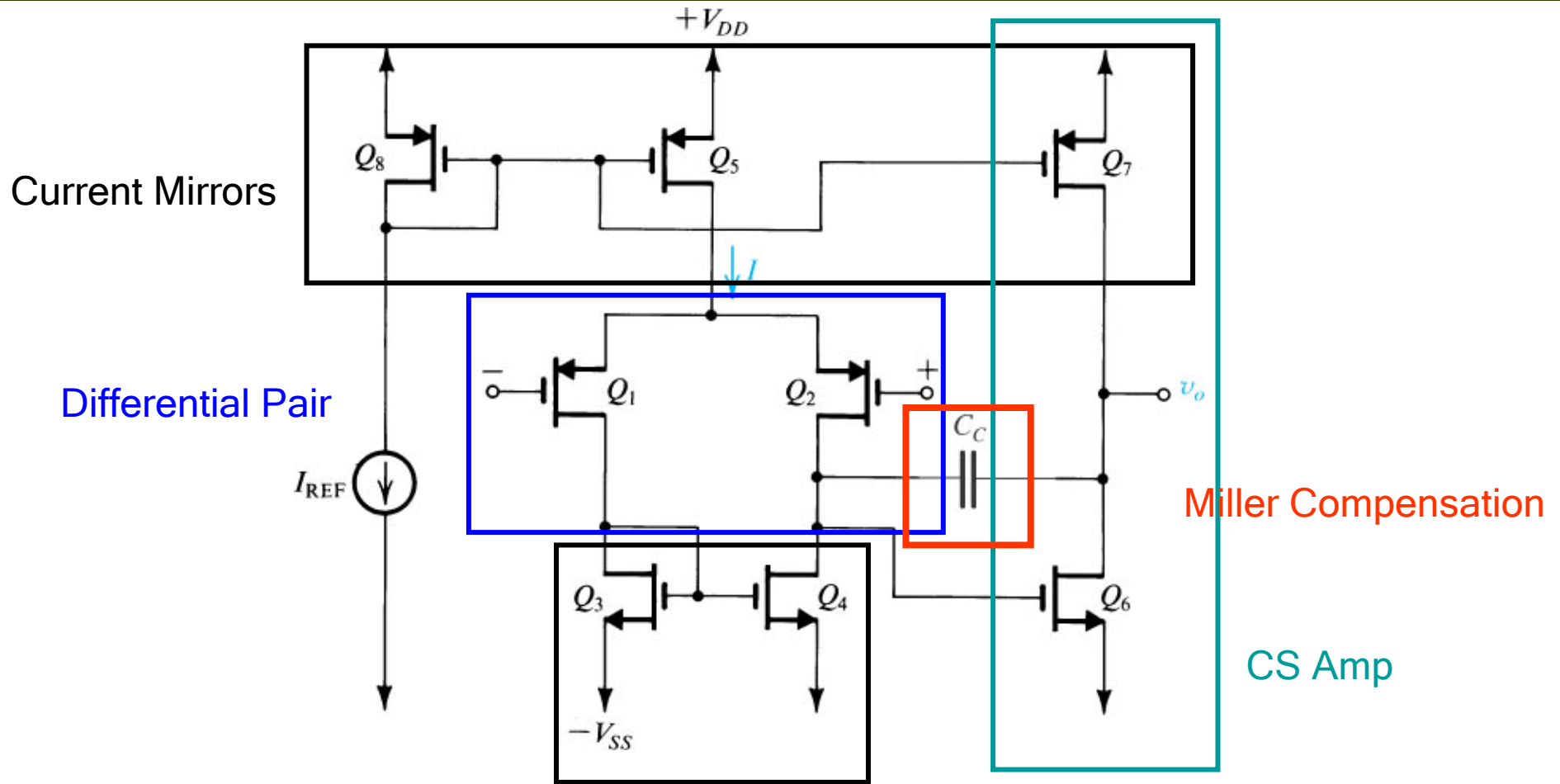



Lect. 12: Two-Stage OTA (S&S 9.1)



OTA: Operational Transconductance Amplifier → High Output Impedance

Lect. 12: Two-Stage OTA

Input Offset

 

Make it as symmetric as possible!

$$I_3 = I_4 = I/2$$

$$V_{GS3} \sim V_{GS4} \sim V_{GS6}$$

$$\frac{I/2}{(W/L)_4} \approx \frac{I_6}{(W/L)_6}$$


$$\text{Since } I_6 = I_7 = \frac{(W/L)_7}{(W/L)_5} I,$$

$$\frac{(W/L)_6}{(W/L)_4} = 2 \frac{(W/L)_7}{(W/L)_5}$$

Additional asymmetric factors due to fabrication

Lect. 12: Two-Stage OTA

Input Common-Mode Range

 

Large $I \rightarrow$ Large V_{SG5} , V_{SG1} , V_{GS3}
 \rightarrow Small input CM range

Q_1, Q_2 should be in saturation

$$V_{SD1} > V_{SG1} - |V_{tp}|$$

$$V_{S1} - V_{D1} > V_{S1} - V_{ICM} - |V_{tp}|$$

$$V_{ICM} > V_{D1} - |V_{tp}|$$

$$V_{ICM, \min} = -V_{ss} + V_{GS3} - |V_{tp}|$$

Q_5 should be in saturation

$$V_{SD5} > V_{SG5} - |V_{tp}|$$


$$V_{S5} - V_{D5} > V_{S5} - V_{G5} - |V_{tp}|$$

$$V_{D5} < V_{G5} + |V_{tp}| = V_{DD} - V_{SG5} + |V_{tp}|$$


$$V_{ICM} + V_{SG1} < V_{DD} - V_{SG5} + |V_{tp}|$$

$$V_{ICM, \max} = V_{DD} - V_{SG5} - V_{SG1} + |V_{tp}|$$

Lect. 12: Two-Stage OTA

 

Small Signal Model

 

Voltage Gain (DC)

Two CS amps in cascade

$$G_{m1} = g_{m1} = g_{m2} \text{ (Ignoring Body Effect)}$$

$$R_1 = r_{o2} // r_{o4}$$

$$A_{v1} = -g_{m2} (r_{o2} // r_{o4})$$

$$G_{m2} = g_{m6}$$

$$R_2 = r_{o6} // r_{o7}$$


$$A_{v2} = -g_{m6} (r_{o6} // r_{o7})$$

$$A_v = g_{m2} g_{m6} (r_{o2} // r_{o4}) (r_{o6} // r_{o7})$$

$$R_{in}: \text{infinity}$$

$$R_{out}: r_{o6} // r_{o7}$$

Lect. 12: Two-Stage OTA

 


Frequency Response

$$C_1 = C_{gd2} + C_{db2} + C_{gd4} + C_{db4} + C_{gs6}$$



$$C_2 = C_{db6} + C_{db7} + C_{gd7} + C_L$$

(C_{gd6} is included in C_c)

$C_2 \gg C_1$ since C_L is usually larger

 

Lect. 12: Two-Stage OTA

 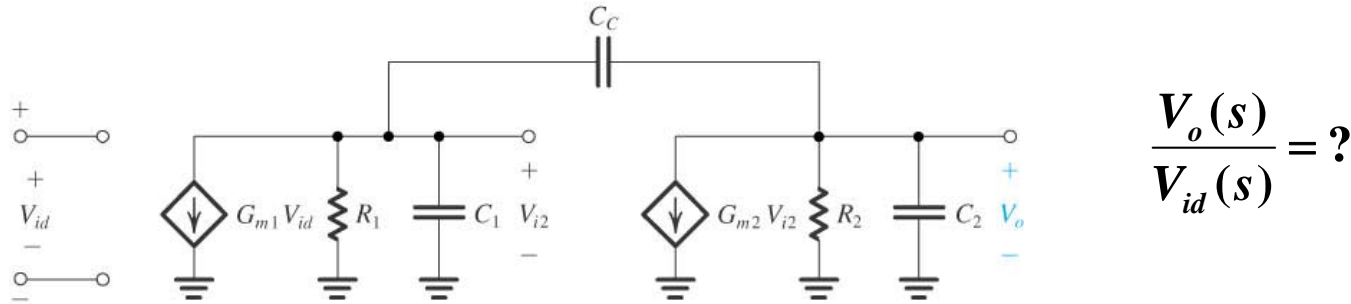


$$\frac{V_o}{V_i} = \frac{(g_m - sC_f)R_2}{1 + s[C_1R_1 + C_2R_2 + C_f(g_mR_1R_2 + R_1 + R_2)] + s^2[C_1C_2 + C_f(C_1 + C_2)]R_1R_2}$$


Since $V_i = G_{m1}V_{id}R_1$, $\frac{V_o(s)}{V_{id}(s)} = G_{m1}R_1 \frac{V_o}{V_i}$ Same Pole-Zero characteristics!

Lect. 12: Two-Stage OTA

In Lect. 9,

 

 
$$\omega_{P1} \approx \frac{1}{C_f g_m R_1 R_2} \quad \omega_{P2} \approx \frac{g_m C_f}{C_1 C_2 + C_f (C_1 + C_2)} \quad \omega_Z = \frac{g_m}{C_f}$$



$$\omega_{P1} \approx \frac{1}{C_C G_{m2} R_1 R_2} \quad \omega_{P2} \approx \frac{G_{m2} C_C}{C_1 C_2 + C_C (C_1 + C_2)} \approx \frac{G_{m2}}{C_2} \quad \omega_Z = \frac{G_{m2}}{C_C}$$

Lect. 12: Two-Stage OTA

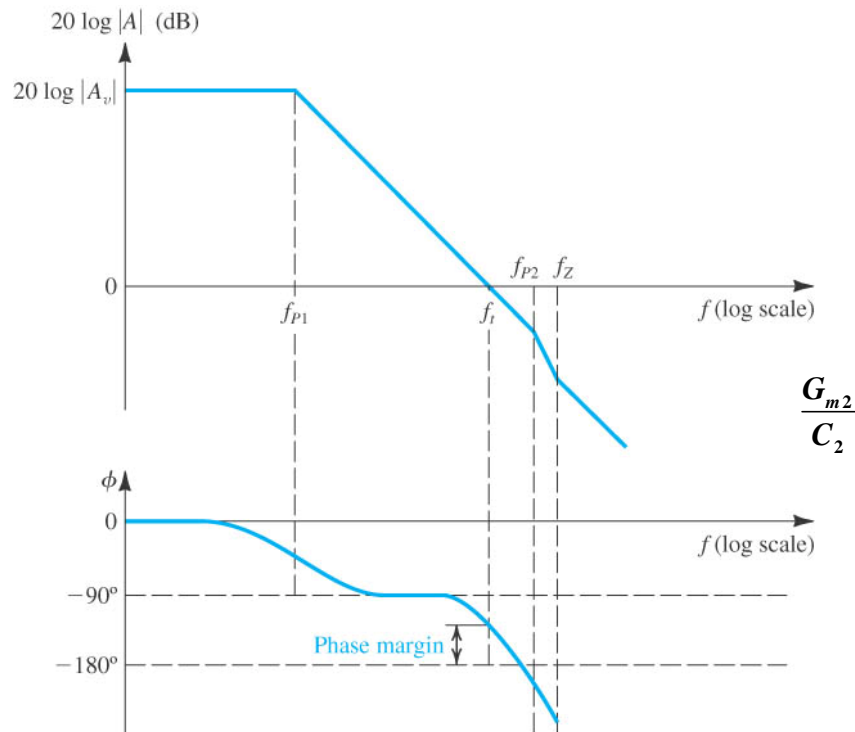Assume we want the following Bode plot so that any amount of feedback is allowed.



$$\omega_{P1} \approx \frac{1}{C_C G_{m2} R_1 R_2}$$

$$\omega_{P2} \approx \frac{G_{m2}}{C_2}$$

$$\omega_Z = \frac{G_{m2}}{C_C}$$


$$\omega_{P1} < \omega_t < \omega_{P2}, \omega_Z$$

$$\begin{aligned} \omega_t &= |A_v| \omega_{P1} \\ &\approx G_{m1} G_{m2} R_1 R_2 \frac{1}{C_C G_{m2} R_1 R_2} = \frac{G_{m1}}{C_C} \end{aligned}$$

$$\omega_t < \omega_{P2} \implies \frac{G_{m1}}{C_C} < \frac{G_{m2}}{C_2}$$

$$\omega_t < \omega_Z \implies \frac{G_{m1}}{C_C} < \frac{G_{m2}}{C_C} \implies G_{m1} < G_{m2}$$

Lect. 12: Two-Stage OTA

 

$$\omega_{P1} \approx \frac{1}{C_C G_{m2} R_1 R_2}$$

$$\omega_{P2} \approx \frac{G_{m2}}{C_2}$$

$$\omega_Z = \frac{G_{m2}}{C_C}$$




More phase margin is possible with a resistor in series with C_C

→ Different Pole-Zero characteristics (Project #2)!

Lect. 12: Two-Stage OTA

Slew Rate


What does the circuit do?

  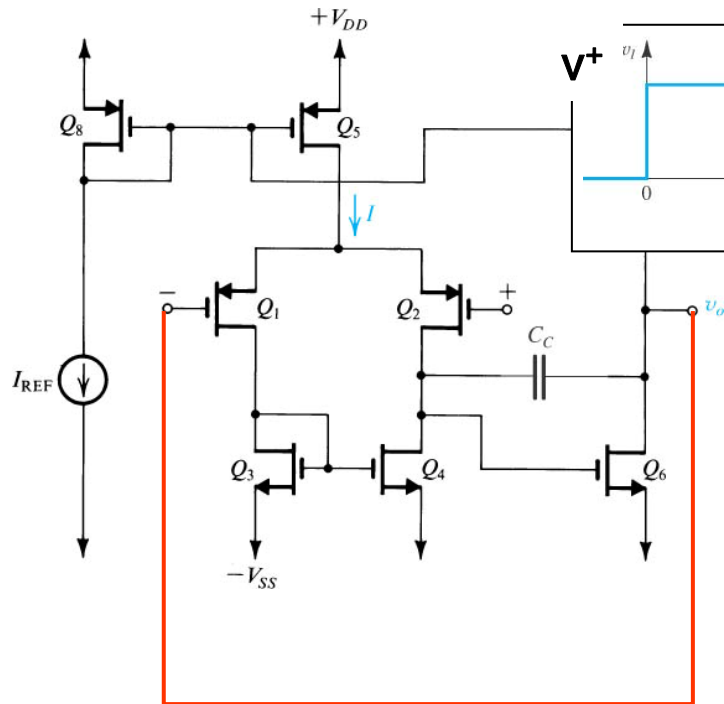

Apply step input at $v^+ \rightarrow v_o(t)=?$

Q_2 off \rightarrow I through $Q_1, Q_3 \rightarrow$ I through C_C


$$v_o(t) = \frac{I}{C_C} t$$

 


Slew Rate: Maximum rate of v_o change $SR = \left. \frac{dv_o}{dt} \right|_{\max} = \frac{I}{C_C}$

Lect. 12: Two-Stage OTA

Slew Rate

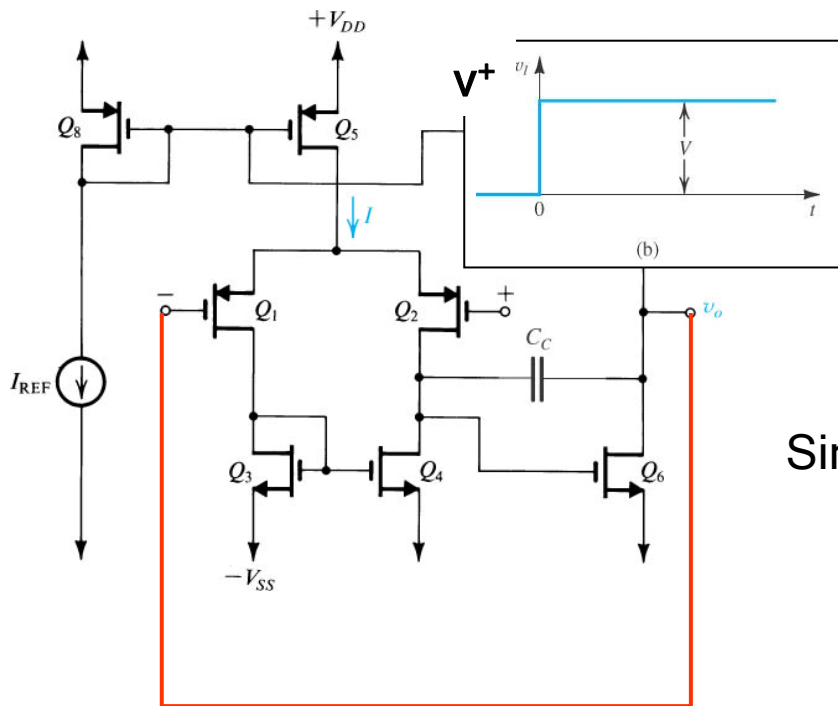

$$v_o(t) = \frac{I}{C_C} t$$

 

$$SR = \frac{I}{C_C}$$

Since $\omega_t \approx \frac{G_{m1}}{C_C}$ and $G_{m1} = g_{m1} = \frac{2I_{D1}}{V_{GS1} - V_T} = \frac{I}{V_{GS1} - V_T}$

For same \$I\$ and \$W/L\$,
PMOS has larger \$(V_{GS1} - V_T)\$

→ Larger \$SR\$

→ Smaller \$G_{m1}\$

$$\therefore SR = \frac{I}{C_C} = \frac{G_{m1}(V_{GS1} - V_T)}{C_C} = \omega_t (V_{GS1} - V_T)$$

Many design trade-offs!