



[P-channel power-MOSFET driver uses unity-gain op amp](#)

[Suded Emmanuel](#) - January 21, 2010

PDF Version

P-channel MOSFETs can simplify designs when you use them as high-side switches on circuits with voltages exceeding 100V dc. When driving a MOSFET, you must rapidly charge and discharge the input capacitance between its gate and its source to reduce heat losses. The circuit in **Figure 1** can accomplish that task. Q_7 , an [International Rectifier](#) IRF5305 power P-channel MOSFET, switches 50V to a load. A series of pulses from a pulse generator or PWM (pulse-with-modulation) source drives the load at frequencies as high as 60 kHz with a variable duty cycle. The circuit comprises Q_4 , R_5 , D_2 , R_4 , D_3 , and R_3 ; provides a means of level-shifting; and ensures that the voltage drop between the gate-to-source voltage of Q_7 never exceeds 10V. When Q_4 is on, 10V develops across D_3 . This voltage drop turns on Q_7 through op amp IC_{1A} , one-half of an MC33072 from [On Semiconductor](#). IC_{1A} has a 13V/ μ sec slew rate and can drive capacitances as high as 10 nF.

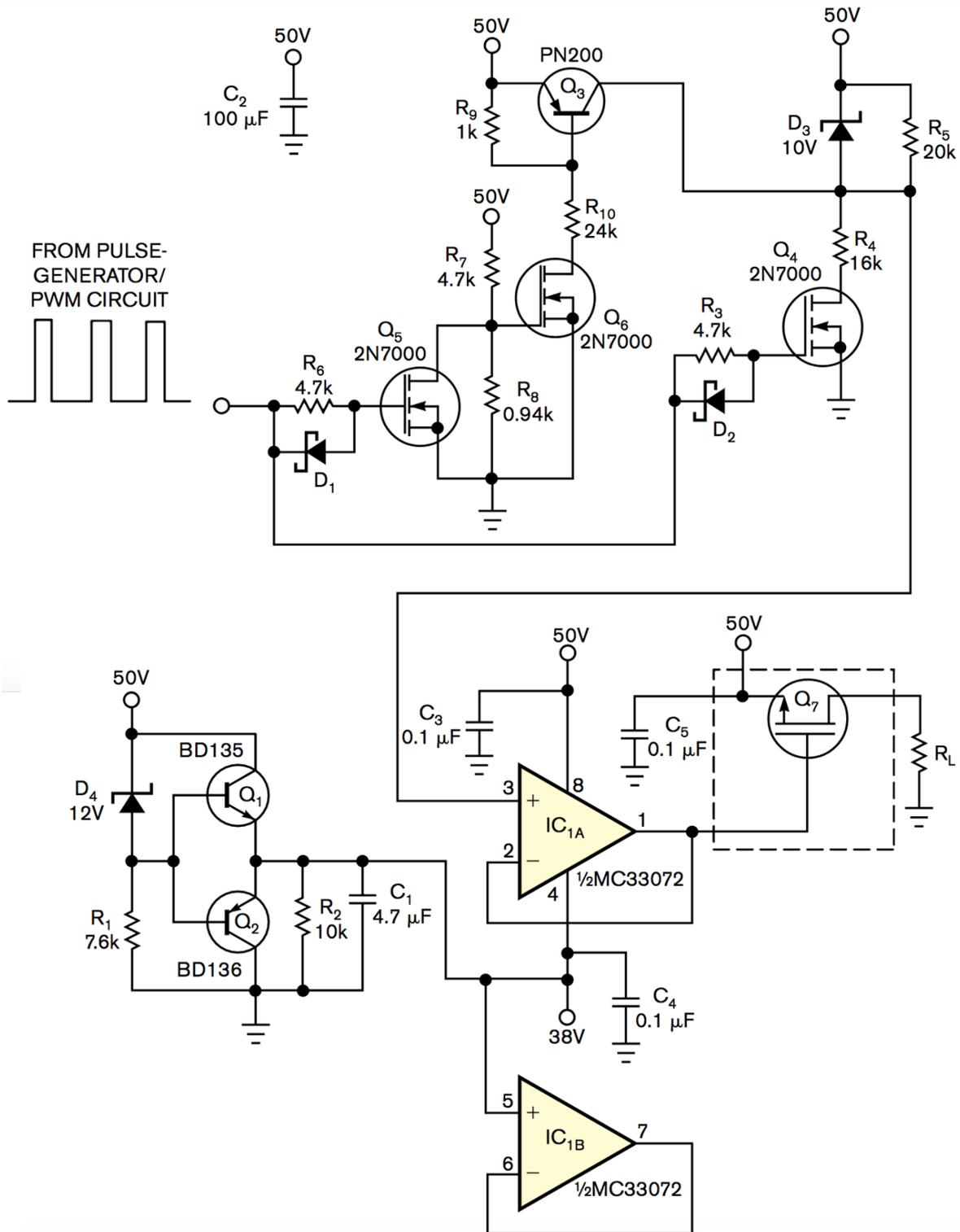


Figure 1 An op amp operating at 38 to 50V provides power to a load through power-MOSFET Q₇.

The combination of D₄, R₁, Q₁, Q₂, R₂, and C₁ provides “ground” for the op amp, which is at 38V—that is, 12V below the 50V rail voltage. The positive voltage is 50V, and ground is 38V. The anode of D₃ connects to the noninverting input of IC_{1A}, whose output drives Q₇'s gate at 40V, which is 10V below the rail voltage of 50V. The circuit comprising R₆, Q₅, D₁, R₇, R₈, Q₆, R₉, R₁₀, and Q₃ rapidly switches D₃'s anode to 50V, which turns off Q₇. Transistor Q₅ functions as an inverter that turns on Q₆, which subsequently drives Q₃ to rapidly switch D₃'s anode to 50V and thus drives Q₇'s gate. Schottky diodes D₁ and D₂ alternately enhance the switching speed of Q₅ and Q₄.

Unity-gain op amp IC_{1A}, with its high slew rate, fast settling, capacitive-driving capability, and feedback of the gate voltage, enhances Q₇'s switching speed. Using this circuit, you can achieve a rise time and fall time of approximately 500 nsec at Q₇'s output.



Related articles:

- [Comparator directly controls power-MOSFET gate](#)
- [Design Ideas Submission Guide](#)