

---

## Designing Operational Amplifier Oscillator Circuits For Sensor Applications

---

*Author: Jim Lepkowski  
Microchip Technology Inc.*

### INTRODUCTION

Operational amplifier (op amp) oscillators can be used to accurately measure resistive and capacitive sensors. Oscillator design can be simplified by using the procedure discussed in this application note. The derivation of the design equations provides a method to select the passive components and determine the influence of each component on the frequency of oscillation. The procedure will be demonstrated by analyzing two state-variable RC op-amp oscillator circuits.

### SENSOR APPLICATIONS

State-variable oscillators are often used in sensor conditioning applications because they have a reliable start-up and a low sensitivity to stray capacitance. The absolute and ratio state-variable oscillators can be used to accurately detect both resistive and capacitive sensors. However, this application note will only analyze capacitive applications. The state-variable's three op-amp topology provides for a more dependable oscillation start-up than a single op amp oscillator. The virtual ground voltage at the inverting terminal of the amplifiers provides for immunity from stray capacitance, which is important in sensor applications, because the sensor capacitance is often only 10 to 100 pF. In addition, the state-variable oscillator does not require matched capacitors or capacitors that have a terminal connected to ground.


The absolute oscillator provides an output frequency that is proportional to the square root of the product of two capacitors (i.e.,  $\text{freq.} \propto (C_1 \times C_2)^{1/2}$ ). Absolute quartz pressure sensors and humidity sensors are examples of capacitive sensors that can use the absolute oscillator. Also, this circuit can be used with resistive sensors, such as RTDs, to provide a temperature-to-frequency conversion.

The ratio oscillator provides an output frequency that is proportional to the square root of the ratio of two capacitors (i.e.,  $\text{freq.} \propto (C_4 / C_3)^{1/2}$ ). The ratio oscillator can be used to cancel the effect of a fluid-level sensor with a varying dielectric constant, such as an oil level sensor. An oil level sensor consists of two capacitances that are formed by tubes where the fluid serves as the dielectric media. The measurement capacitor ( $C_{\text{MEAS}}$ ) is partially covered by fluid and detects the level of the oil in the tank. In contrast, the compensation sensor ( $C_{\text{COMP}}$ ) is completely buried in the fluid. When the ratio  $C_{\text{MEAS}} / C_{\text{COMP}}$  is calculated, the dielectric constant of the oil is canceled. Air pressure and acceleration sensors can also use the ratio sensor to minimize the error that occurs from the variance of the dielectric constant over temperature.

### TRANSDUCER SYSTEM

A block diagram of a typical sensor system is shown in Figure 1. The oscillation frequency can be found by counting the number of clock pulses (i.e., MHz) in a time window that is formed by the square wave output (i.e., kHz) of a comparator circuit. The counter and comparator circuits can be implemented with a PICmicro<sup>®</sup> microcontroller.

The PICmicro microcontroller can be used to provide curve-fit temperature correction for precision sensing applications. Temperature correction can be accomplished by implementing a curve-fitting routine with data obtained by calibrating the sensor over the operating range. The temperature correction data can be stored in the E<sup>2</sup> memory of the PICmicro microcontroller. A silicon IC sensor can provide the temperature of the sensor.

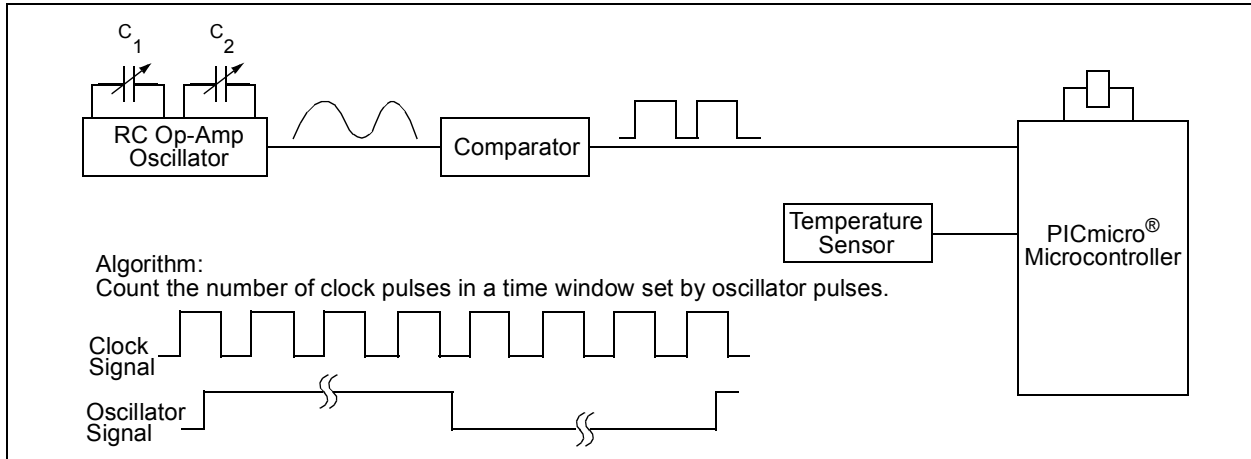

**FIGURE 1:** Typical RC Operational Amplifier Oscillator Sensor System.

## OSCILLATOR THEORY

An oscillator is a positive feedback control system that generates an output without requiring an input signal. A sustained oscillation is initiated by factors such as noise pick-up or power supply transients. Figure 2 shows a block diagram of an oscillator, along with the definition of the mathematical terms that describe an oscillator.

The design equations of an oscillator are determined by analyzing the denominator of the transfer equation  $T(s)$  of the circuit. The poles of the denominator of  $T(s)$ , or equivalently, the zeroes of the characteristic equation ( $\Delta s$ ), determine the time domain behavior and stability of the system. An oscillator is on the border line between a stable and an unstable system and is formed when a pair of poles are on the imaginary axis.


The magnitude and phase equations of an oscillator also must be analyzed. If the magnitude of the loop-gain is greater than one and the phase is zero, the amplitude of oscillation will increase exponentially until a factor in the system, such as the supply voltage, restricts the growth. In contrast, if the magnitude of the loop-gain is less than one, the amplitude of oscillation will exponentially decrease to zero.

## OSCILLATOR DESIGN PROCEDURE

Listed below is a procedure to design RC operational amplifier oscillators. Refer to the design equation section of this application note for additional information on deriving oscillator design equations.

### Step 1: Find LG and $\Delta s$

The oscillation frequency is determined by finding the poles of the denominator of the transfer equation  $T(s)$ , or equivalently, the zeroes of the numerator  $N(s)$  of the characteristic equation ( $\Delta s$ ). Mason's Reduction Theorem, shown in Appendix A, provides a method of obtaining  $\Delta s$ . Then  $\Delta s$  is found by breaking the feedback loop and obtaining the gain equation at each op-amp in order to calculate the loop-gain.

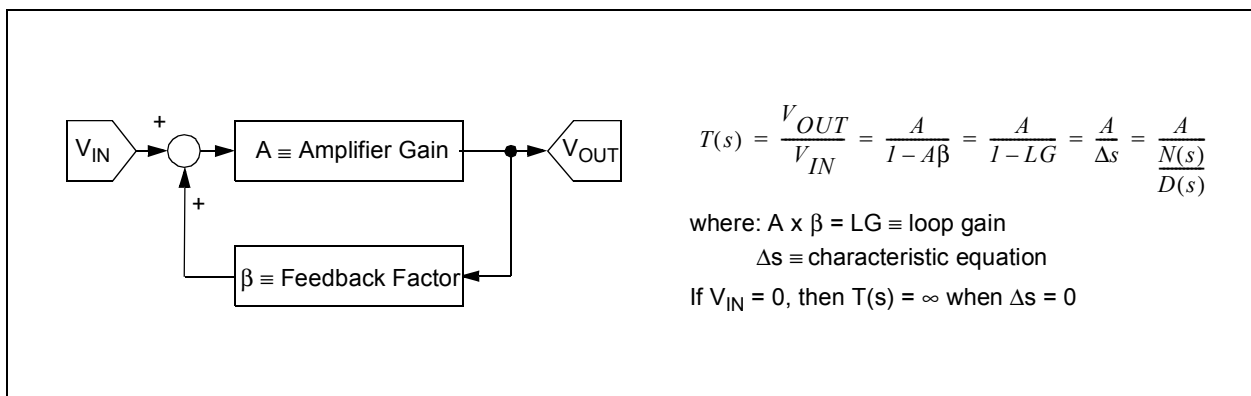

**FIGURE 2:** Oscillator Block Diagram.

**Step 2: Solve  $N(s) = 0$** 

The second step in the procedure determines the zeroes of  $N(s)$ . Routh's stability criterion, shown in Appendix B, provides a method that determines the zeroes of the characteristic equation without the necessity of factoring the equation.

First, the Routh test consists of forming a coefficient array from  $N(s)$ . Next, the procedure substitutes  $s = j\omega_o$  for  $s$ , with the summation of the row set to zero. If the row equation produces a non-trivial solution for  $\omega_o$ , the procedure is complete and the frequency of oscillation is equal to  $\omega_o$ . If the row equation does not yield an equation that can be solved for  $\omega_o$ , the procedure continues with the next row in the Routh array. Usually, it is necessary only to complete the first two or three rows of the Routh array to produce an equation that can be solved for  $\omega_o$ .

**Step 3: Sub-Circuit Design Equations**

The third step in the design procedure analyzes the sub-circuits formed at each amplifier. The sub-circuit equations are formed by obtaining the gain equation and pole/zero locations for each amplifier.

**Step 4: Verify  $|LG| \geq 1$** 

The final step in the procedure verifies that the loop-gain is equal to, or greater than, one after the R and C component values have been chosen. This step is also required to verify that the amplifiers do not saturate, which will result in an error in the oscillation frequency.

**AMPLIFIER SELECTION CRITERIA**

The appropriate op amp to use in a sensor oscillator is determined by the required accuracy and acceptable distortion of the oscillation frequency. The design equations assume that the amplifiers are ideal. However, op amps have a finite gain bandwidth product (GBW), a limited slew rate (SR) and full power bandwidth ( $f_p$ ). The non-ideal characteristics of the amplifier will lower the oscillation frequency at high frequencies and may also result in a design with poor start-up characteristics. Note that the total harmonic distortion specification of the amplifiers is critical for oscillators that are used as sine wave references. However, the shape of the waveform is not critical in most sensor applications because only the frequency of the output is measured.

Several general design rules can be used to select an op amp for an oscillator circuit. First, the GBW should be a factor of 10 to 100 higher than the maximum oscillation frequency. Next, the full-power bandwidth, defined as  $f_p = SR / (2\pi V_p)$ , where  $V_p$  is the voltage swing ( $V_{O(max)} - V_{O(min)}$ ) of the output signal, should be at least 2 times greater than the maximum oscillation frequency. For example, the MCP6024 quad amplifier has a GBW = 10 MHz (typ.), SR = 7 V/ $\mu$ s (typ.) and a  $f_p$  of 400 kHz, with  $V_{DD} = 5V$ . An oscillator with a maximum frequency of 100 kHz can be implemented

with the MCP6024 with enough design margin that the non-ideal characteristics of the amplifier can be neglected.

**ABSOLUTE STATE-VARIABLE OSCILLATOR****Circuit Description**

The schematic of the absolute circuit is shown in Figure 3. The state-variable oscillator consists of two integrators and an inverter circuit. Each integrator provides a phase shift of  $90^\circ$ , while the inverter adds an additional  $180^\circ$  phase shift. The total phase shift of  $360^\circ$  of the feedback loop produced by the three amplifiers results in the oscillation. The first integrator stage consists of amplifier  $A_1$ , resistor  $R_1$  and sensor capacitance  $C_1$ . The second integrator consists of amplifier  $A_2$ , resistor  $R_2$  and sensor capacitance  $C_2$ . The inverter stage consists of amplifier  $A_3$ , resistors  $R_3$  and  $R_4$  and capacitor  $C_4$ . The addition of capacitor  $C_4$  helps ensure oscillation start-up by providing an additional phase shift.


The absolute oscillator does not require a limit circuit if rail-to-rail input/output (RRIO) amplifiers are used and the gain of the inverter stage ( $A_3$ ) is equal to one (i.e.,  $R_3 = R_4$ ). The sinewave output of the signal will swing within approximately 50 mV of the  $V_{DD}$  and  $V_{DD}$  power rails as shown in Figure 5.

A complementary output voltage comparator ( $A_4$ ) is used to convert the oscillator's sinewave output to a square wave digital signal. The comparator functions as a zero-crossing detector and the switching point is equal to the virtual ground voltage (i.e.,  $V_{DD}/2$ ). Resistor  $R_9$  is used to provide additional hysteresis ( $V_{HYS}$ ) to the comparator. Listed below is the hysteresis equation.


**EQUATION:**

$$V_{HYS} = \frac{R_8}{R_8 + R_9} \times (V_{O(max)} - V_{O(min)})$$

$$V_{HYS} \cong \frac{R_8}{R_8 + R_9} \times V_{DD}$$

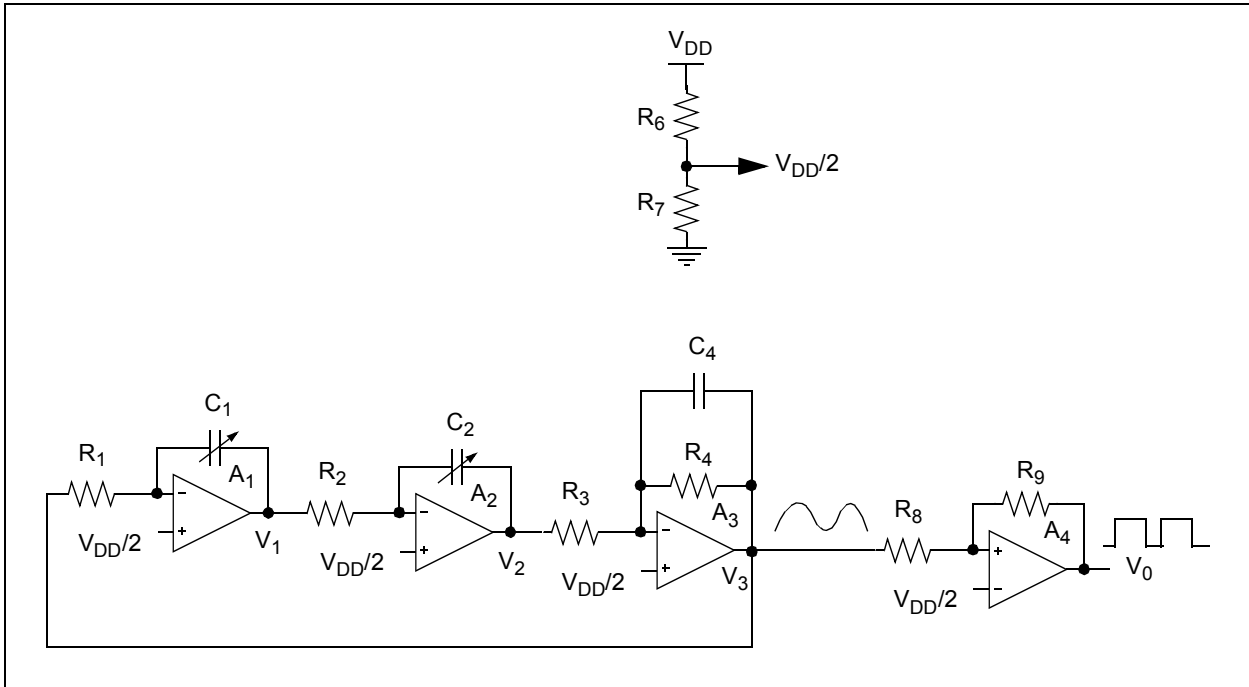

**FIGURE 3:** Absolute Oscillator Schematic.

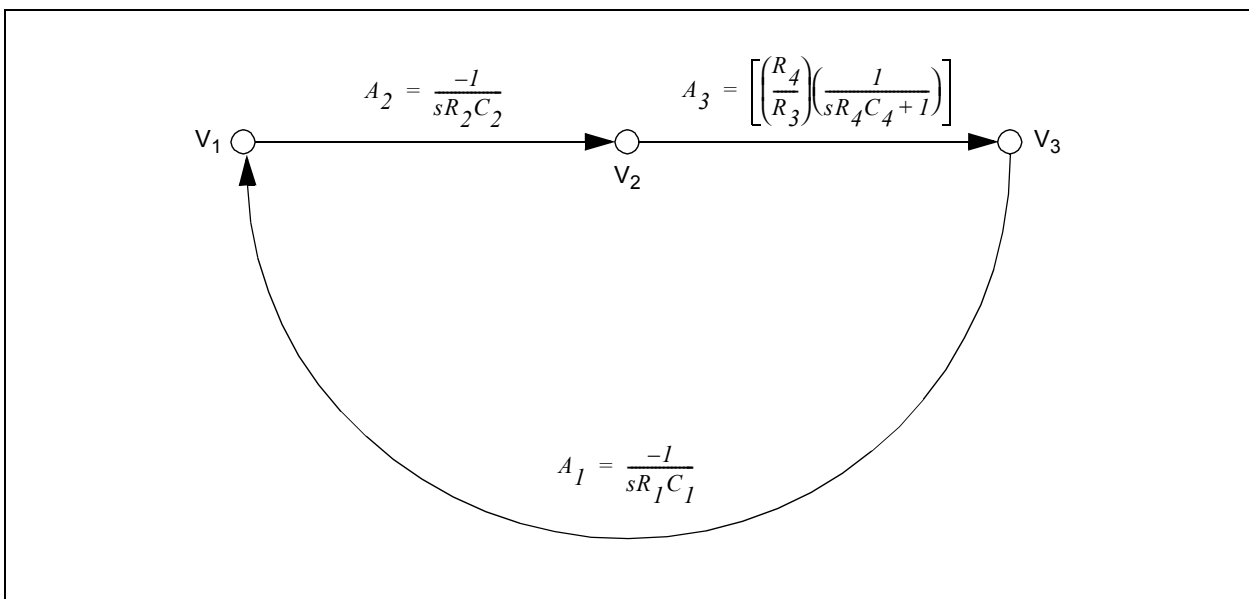

**FIGURE 4:** Absolute Oscillator Signal Flow Diagram.


## ABSOLUTE STATE-VARIABLE

### Design Equations
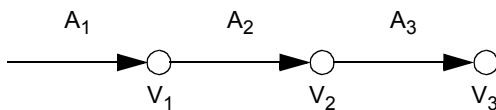
#### STEP 1: FIND LG AND ΔS

$$T(s) = \frac{A}{1-LG} = \frac{A}{\Delta s} = \frac{A}{\frac{N(s)}{D(s)}}$$

The loop-gain is found by breaking the loop in the signal flow diagram of Figure 4, as shown below.



$$\begin{aligned} A_1 &= -1/(sR_1C_1) \\ A_2 &= -1/(sR_2C_2) \\ A_3 &= -Z_4/Z_3 \\ &= -(R_4 \parallel C_4)/R_3 \\ &= -[(R_4/R_3)(1/(sR_4C_4 + 1))] \end{aligned}$$

$$\begin{aligned} LG &= A_1 \times A_2 \times A_3 \\ &= [-1/(sR_1C_1)][-1/(sR_2C_2)][-(R_4/R_3)(1/(sR_4C_4 + 1))] \\ &= -[R_4/(s^3R_1R_2R_3R_4C_1C_2C_4 + s^2R_1R_2R_3C_1C_2)] \end{aligned}$$

$$\begin{aligned} \Delta s &= N(s)/D(s) = 1 - LG \\ &= 1 - [R_4/(s^3R_1R_2R_3R_4C_1C_2C_4 + s^2R_1R_2R_3C_1C_2)] \\ &= \frac{[s^3R_1R_2R_3R_4C_1C_2C_4 + s^2R_1R_2R_3C_1C_2 + R_4]}{[s^3R_1R_2R_3R_4C_1C_2C_4 + s^2R_1R_2R_3C_1C_2]} \end{aligned}$$

$$N(s) = s^3R_1R_2R_3R_4C_1C_2C_4 + s^2R_1R_2R_3C_1C_2 + R_4$$

#### STEP 2: SOLVE N(s) = 0

The zeros of the characteristic equation are determined by using the Routh stability test.

$$\begin{aligned} N(s) &= a_0s^3 + a_1s^2 + a_2s + a_3 \\ a_0 &= R_1R_2R_3R_4C_1C_2C_4 \\ a_1 &= R_1R_2R_3C_1C_2 \\ a_2 &= 0 \\ a_3 &= R_4 \end{aligned}$$

Routh Stability Test Coefficient Array

$$\begin{aligned} \text{row } s^3 & \quad a_0 + a_2 = 0 \\ \text{row } s^2 & \quad a_1 + a_3 = 0 \end{aligned}$$

Row  $s^3$  produces a trivial solution ( $\omega_0 = 0$ ):

$$a_0(j\omega_0)^3 + 0 = 0$$

The procedure continues by analyzing row  $s^2$  to determine when the equation is equal to zero.

Let  $s = j\omega_0$

$$a_1s^2 + a_3 = (R_1R_2R_3C_1C_2)(j\omega_0)^2 + R_4 = 0$$

$$0 = R_4 - R_1R_2R_3C_1C_2\omega_0^2$$

$$\omega_0^2 = [R_4/(R_1R_2R_3C_1C_2)]$$

$$\omega_0 = [R_4/(R_1R_2R_3C_1C_2)]^{1/2}$$

$$P = 2\pi/\omega_0 = 2\pi/[R_4/(R_1R_2R_3C_1C_2)]^{1/2}$$

Note that  $C_4$  does not appear in the oscillation equation.  $C_4$  and  $R_4$  form a low-pass filter. The gain of amplifier  $A_3$  will not be a function of  $C_4$  if the oscillation frequency is less than the cut-off frequency of the filter.

If:

1.  $R_1 = R_2 = R$
2.  $C_1 = C_2 = C$
3.  $R_3 = R_4$

Then:

$$P = 2\pi RC$$

#### STEP 3: SUB-CIRCUIT DESIGN EQUATIONS

Integrator  $A_1$

$$\text{Gain } A_1 = -1/(2\pi fR_1C_1)$$

$$\text{Pole } f_{p1} = 1/(2\pi R_1C_1)$$

Integrator  $A_2$

$$\text{Gain } A_2 = -1/(2\pi fR_2C_2)$$

$$\text{Pole } f_{p2} = 1/(2\pi R_2C_2)$$

Integrator  $A_3$

$$\text{Gain} = -[(R_4/R_3)(1/(sR_4C_4 + 1))]$$

$$\text{Gain} \cong -R_4/R_3$$

#### STEP 4: VERIFY $|LG| \geq 1$

Assume:

1.  $R_1 = R_2 = R$
2.  $C_1 = C_2 = C$
3.  $R_3 = R_4$

$$|A_1| = |A_2| = |A_3| = 1$$

$$LG = |A_1 \times A_2 \times A_3| = 1$$

$$V_1 = |A_1 \times V_3|$$

$$V_2 = |A_2 \times V_1|$$

$$V_3 = |A_3 \times V_2|$$

Note that a voltage limit circuit should be added if rail-to-rail input/output operational amplifiers are not used, or if the gain of the inverter is not equal to one (i.e.,  $R_3 \neq R_4$ ). A limit circuit is required to prevent the frequency error that will result from the saturation delay time of the amplifiers.

## ABSOLUTE STATE-VARIABLE

### Test Results


The components used in the evaluation design are listed below. Note that the capacitive sensor (i.e.,  $C_1$  and  $C_2$ ) was simulated with discrete capacitors.

- $R_1 = R_2 = R_6 = R_7 = 32.7 \text{ k}\Omega$
- $R_3 = R_4 = 10 \text{ k}\Omega$
- $R_8 = 1 \text{ k}\Omega$
- $R_9 = 1 \text{ M}\Omega$
- $C_1 = C_2 = \text{see Table 1}$
- $C_4 = 18 \text{ pF}$
- $V_{DD} = 5.0\text{V}$
- $A_1, A_2, A_3 \equiv \text{MCP6024 (quad RRIO, GBW = 10 MHz)}$
- $A_4 \equiv \text{MCP6541 Push-Pull Output Comparator}$

The measured and calculated oscillation frequency is shown in Table 1. Figure 5 shows the oscillation waveform when  $C_1 = C_2 = 220 \text{ pF}$ . The error in the measured oscillation is attributed to the accuracy of the test equipment.

**TABLE 1: ABSOLUTE OSCILLATOR TEST RESULTS**

Capacitor Values	Calculated Oscillation Period (Frequency)	Measured Oscillation Period (Frequency)
$C_1 = C_2 = 47 \text{ pF}$	9.66 $\mu\text{s}$ (103.6 kHz)	10.0 $\mu\text{s}$ (100.0 kHz)
$C_1 = C_2 = 56 \text{ pF}$	11.5 $\mu\text{s}$ (86.9 kHz)	12.0 $\mu\text{s}$ (83.3 kHz)
$C_1 = C_2 = 82 \text{ pF}$	16.9 $\mu\text{s}$ (59.4 kHz)	16.6 $\mu\text{s}$ (60.2 kHz)
$C_1 = C_2 = 100 \text{ pF}$	20.6 $\mu\text{s}$ (48.7 kHz)	21.0 $\mu\text{s}$ (47.6 kHz)
$C_1 = C_2 = 150 \text{ pF}$	30.8 $\mu\text{s}$ (32.6 kHz)	30.0 $\mu\text{s}$ (33.3 kHz)
$C_1 = C_2 = 220 \text{ pF}$	45.2 $\mu\text{s}$ (22.1 kHz)	46.0 $\mu\text{s}$ (21.7 kHz)

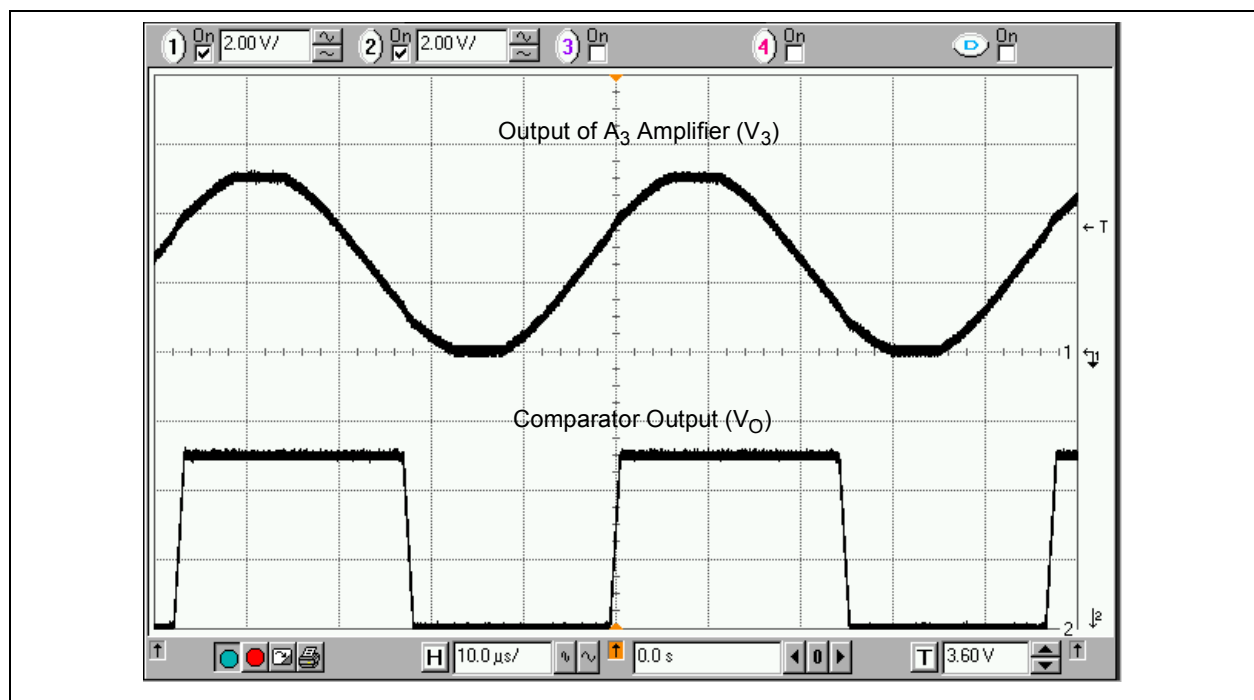


**FIGURE 5:** Absolute Oscillator Test Results ( $C_1 = C_2 = 220 \text{ pF}$ ).

## RATIO STATE-VARIABLE OSCILLATOR


### Circuit Description

The schematic of the ratio circuit is shown in Figure 6. This circuit consists of two integrators and a differentiator circuit. The integrators formed by amplifiers  $A_1$  and  $A_2$  are identical to the integrators used in the absolute circuit. The differentiator stage is formed by amplifier  $A_3$ , resistors  $R_3$ ,  $R_4$  and  $R_5$ , and the sensor capacitors  $C_3$  and  $C_4$  to provide a  $180^\circ$  phase shift. The comparator ( $A_4$ ) used to convert the sinewave output to a square wave digital signal is identical to the absolute oscillator circuit.


A Bode plot of the differentiator stage is provided in Figure 8. The values of resistors  $R_3$ ,  $R_4$  and  $R_5$  are selected to set the break frequencies of the differentiator stage so that the gain of the stage is equal to  $-C_3/C_4$  at the oscillation frequency. Resistor  $R_5$  is also used to provide a DC current path around capacitor  $C_3$  in order to initiate oscillation at power-up.

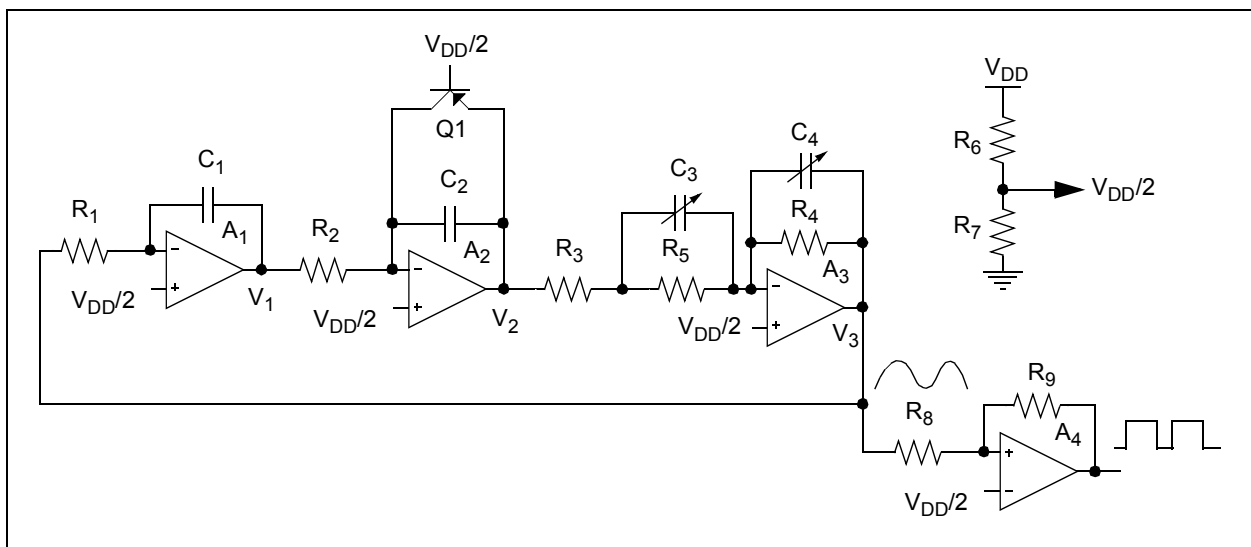

**FIGURE 6:** Ratio Oscillator Schematic.

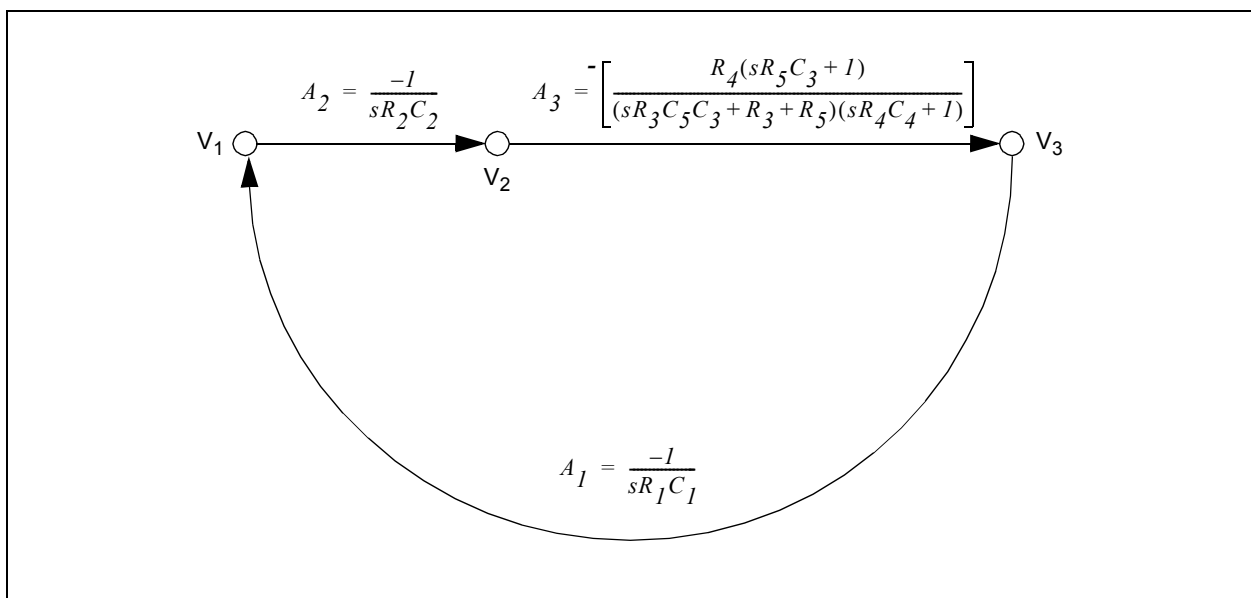

**FIGURE 7:** Ratio Oscillator Signal Flow Diagram.

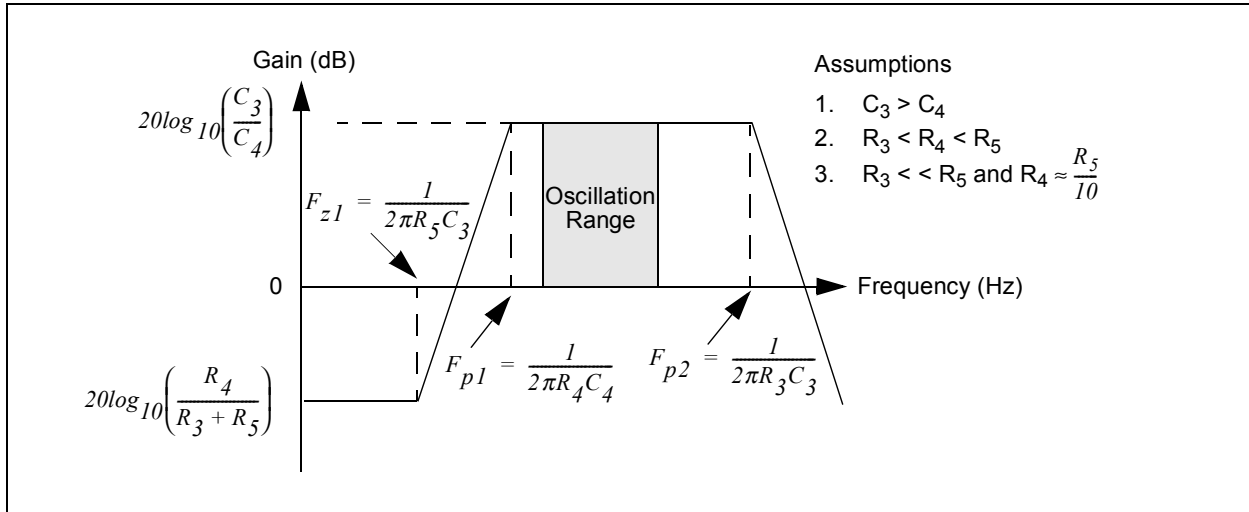

**FIGURE 8:** Bode Plot of Differentiator Amplifier.

### Voltage Limit Circuit

The ratio oscillator uses a limit circuit to accommodate the varying gain requirement of the circuit. It may be necessary to add a voltage limit or clamp circuit to the oscillator to prevent the amplifiers from saturating and avoid slew rate limitations. The voltage limit circuit formed by PNP transistor  $Q_1$  is used to create the maximum voltage limit. The clamping voltage of the limit circuit is provided below:

#### EQUATION:

$$V_{Max\_Limit} = V_{Q1\_base} + V_{Q1\_base-to-emitter}$$

$$V_{Max\_Limit} \cong V_{Q1\_base} + 0.7V$$

In single-supply applications, it is not necessary to use both maximum and minimum limit circuits. Only one of the limit circuits is required due to the symmetry of the sinewave that is centered around the virtual ground voltage at the non-inverting terminal of the amplifiers ( $V_{DD}/2$ ). In the reference design of Figure 6,  $V_{DD}$  is equal to 5V and  $V_{Q1\_base}$  is equal to 2.5V. Thus, the oscillation waveform at  $V_2$  will swing from 1.8V to 3.2V or  $2.5V \pm 0.7V$ .

Note that the transistor adds a small capacitance ( $C_{Q1}$ ) to the integrator capacitor of the circuit ( $C_2$ ). If  $C_2$  is relatively small, the effective capacitance of the limit circuit ( $C_{Limit}$ ) can be reduced by connecting a diode in series between the emitter junction and the output of the amplifier (i.e.  $1/C_{Limit} = 1/C_{Q1} + 1/C_{Diode}$ ).




## RATIO STATE-VARIABLE

### Design Equations
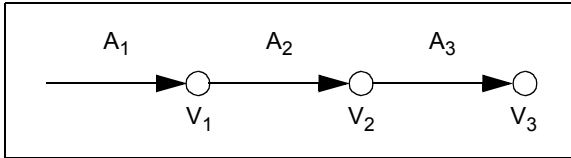
#### STEP 1: FIND LG AND ΔS

$$T(s) = \frac{A}{1-LG} = \frac{A}{\Delta s} = \frac{A}{\frac{N(s)}{D(s)}}$$

The loop-gain is found by breaking the loop in the signal flow diagram of Figure 7, as shown below.



$$\begin{aligned} A_1 &= -1/(sR_1C_1) \\ A_2 &= -1/(sR_2C_2) \\ A_3 &= Z_4/Z_3 \\ &= -[(R_4 \parallel C_4)/(R_3 + (R_5 \parallel C_3))] \\ &= -[R_4(sR_5C_3 + 1)/(sR_3R_5C_3 + R_3 + R_5)(sR_4C_4 + 1)] \end{aligned}$$

LG = A<sub>1</sub> × A<sub>2</sub> × A<sub>3</sub>:

$$\begin{aligned} LG &= [-1/(sR_1C_1)][-1/(sR_2C_2)] \left[ \frac{[-R_4(sR_5C_3 + 1)]}{(sR_3R_5C_3 + R_3 + R_5)(sR_4C_4 + 1)} \right] \\ &= \left[ \frac{-(sR_4R_5C_3 + R_4)/s^4 R_1R_2R_3R_4C_1C_2C_3C_4 + s^3 ((R_1R_2C_1C_2)(R_3R_5C_3 + R_3R_4C_4 + R_4R_5C_4)) + s^2 (R_1R_2C_1C_2)(R_3 + R_5)}{(sR_3R_5C_3 + R_3 + R_5)(sR_4C_4 + 1)} \right] \end{aligned}$$

Δs = N(s) / D(s) = 1 - LG:

$$\Delta s = \frac{\left[ (s^4 R_1R_2R_3R_4R_5C_1C_2C_3C_4 + s^3 (R_1R_2C_1C_2)(R_3R_5C_3 + R_3R_4C_4 + R_4R_5C_4)) + s^2 (R_1R_2C_1C_2)(R_3 + R_5) + sR_4R_5C_3 + R_4 \right]}{\left[ (s^4 R_1R_2R_3R_4R_5C_1C_2C_3C_4) + s^3 ((R_1R_2C_1C_2)(R_3R_5C_3 + R_3R_4C_4 + R_4R_5C_4)) + s^2 (R_1R_2C_1C_2)(R_3 + R_5) \right]}$$

#### STEP 2: SOLVE N(s) = 0

The zeroes of the characteristic equation are determined by using the Routh stability test:

$$\begin{aligned} Ns &= a_0s^4 + a_1s^3 + a_2s^2 + a_3s + a_4 \\ a_0 &= R_1R_2R_3R_4R_5C_1C_2C_3C_4 \\ a_1 &= (R_1R_2C_1C_2)(R_3R_5C_3 + R_3R_4C_4 + R_4R_5C_4) \\ a_2 &= (R_1R_2C_1C_2)(R_3 + R_5) \\ a_3 &= R_4R_5C_3 \\ a_4 &= R_4 \end{aligned}$$

Routh Stability Test Coefficient Array

row s<sup>4</sup> a<sub>0</sub> + a<sub>2</sub> + a<sub>4</sub> = 0

row s<sup>3</sup> a<sub>1</sub> + a<sub>3</sub> = 0

Row s<sup>4</sup> produces an equation that cannot be solved with simple algebra. Therefore, the next row is analyzed:

$$a_0(j\omega_0)^4 + a_2(j\omega_0)^2 + a_4 = 0$$

The procedure continues by analyzing row  $s^3$  to determine when the row equation is equal to zero.

$$a_1 s^3 + a_3 s = s(a_1 s^2 + a_3) = 0$$

Let  $s = j\omega_o$

$$j\omega_o(-a_1 \omega_o^2 + a_3) = 0$$

$$\omega_o^2 = \frac{a_3}{a_1}$$

$$= \frac{R_4 R_5 C_3}{(R_1 R_2 C_1 C_2)(R_3 R_5 C_3 + R_3 R_4 C_4 + R_4 R_5 C_4)}$$

$$\omega_o = \left[ \frac{(R_4 R_5 C_3)}{(R_1 R_2 C_1 C_2)(R_3 R_5 C_3 + R_3 R_4 C_4 + R_4 R_5 C_4)} \right]^{1/2}$$

If:

1.  $R_1 = R_2 = R$
2.  $C_1 = C_2 = C$

Then:

$$P = \frac{2\pi}{\omega_o}$$

$$P = 2\pi RC \left[ \frac{R_3 C_4}{R_5 C_3} + \frac{C_4}{C_3} + \frac{R_3}{R_4} \right]^{1/2}$$

If:

1.  $R_5 \gg R_3$
2.  $R_4 \gg R_3$

Then:

$$P \cong 2\pi RC \left[ \frac{C_4}{C_3} \right]^{1/2}$$

## STEP 3: SUB-CIRCUIT DESIGN EQUATIONS

Integrator  $A_1$

$$\text{Gain } A_1 = -1/(2\pi f R_1 C_1)$$

$$\text{Pole } f = 1/(2\pi R_1 C_1)$$

Integrator  $A_2$

$$\text{Gain } A_2 = -1/(2\pi f R_2 C_2)$$

$$\text{Pole } f = 1/(2\pi R_2 C_2)$$

Differentiator  $A_3$

$$\text{DC Gain} = -R_4/(R_3 + R_5)$$

$$\text{Gain at Oscillation} = -\frac{C_3}{C_4}$$

$$\text{Pole } f_{p1} = 1/(2\pi R_4 C_4)$$

$$\text{Pole } f_{p2} = 1/(2\pi R_3 C_3)$$

$$\text{Zero } f_z = 1/(2\pi R_5 C_3)$$

## STEP 4: VERIFY $|LG| \geq 1$

Assume:

1.  $R_5 \gg R_3$  and  $R_4 \gg R_3$ , then  $A_3 = -C_3/C_4$
2.  $V_2 = V_{Max\_Limit}$  (i.e. place limit circuit at  $A_2$ )

Next, calculate the voltages at the output of each amplifier starting at  $V_2$ .

$$V_2 = V_{Max\_Limit}$$

$$V_3 = |A_3 \times V_2| = \left| \frac{C_3}{C_4} \times V_{Max\_Limit} \right|$$

$$V_1 = |A_1 \times V_3| = \left| \frac{1}{2\pi f R_1 C_1} \times V_3 \right|$$

Oscillation will be sustained if:

$$|A_2 \times V_1| \geq V_{Max\_Limit}$$

$$\left| \left[ \left( \frac{1}{2\pi f R_2 C_2} \right) \times V_1 \right] \right| \geq V_{Max\_Limit}$$

## RATIO STATE-VARIABLE


### Test Results

$R_1 = R_2 = R_6 = R_7 = 32.7 \text{ k}\Omega$   
 $C_1 = C_2 = 220 \text{ pF}$   
 $C_3 = C_4 = \text{see Table 2}$   
 $R_3 = 5 \text{ k}\Omega$   
 $R_4 = 3.3 \text{ M}\Omega$   
 $R_5 = 10 \text{ M}\Omega$   
 $R_8 = 1 \text{ k}\Omega$   
 $R_9 = 1 \text{ M}\Omega$   
 $V_{DD} = 5.0 \text{ V}$   
 $A_1, A_2, A_3 \equiv \text{MCP6024 (quad RRIO, GBW = 10 MHz)}$   
 $A_4 \equiv \text{MCP6541 Push-Pull Output Comparator}$   
 $Q_1 \equiv 2\text{N}3906$

The measured and calculated oscillation frequency is shown in Table 2. Figure 9 shows the oscillation waveform when  $C_3 = 100 \text{ pF}$  and  $C_4 = 47 \text{ pF}$ . Note that the voltage limit circuit adds distortion to the waveform of amplifier  $A_2$ . In most sensor applications, waveform distortion is inconsequential because the measurement is proportional to frequency and not the amplitude of the oscillation.

**TABLE 2: RATIO OSCILLATOR TEST RESULTS**

Capacitor Values	Calculated Oscillation Period (Frequency)	Measured Oscillation Period (Frequency)
$C_3 = 47 \text{ pF}$ $C_4 = 47 \text{ pF}$	45.2 $\mu\text{s}$ (22.1 kHz)	47.0 $\mu\text{s}$ (21.3 kHz)
$C_3 = 47 \text{ pF}$ $C_4 = 100 \text{ pF}$	65.9 $\mu\text{s}$ (15.2 kHz)	68.0 $\mu\text{s}$ (14.7 kHz)
$C_3 = 47 \text{ pF}$ $C_4 = 220 \text{ pF}$	97.8 $\mu\text{s}$ (10.2 kHz)	98.4 $\mu\text{s}$ (10.2 kHz)
$C_3 = 56 \text{ pF}$ $C_4 = 47 \text{ pF}$	41.4 $\mu\text{s}$ (24.2 kHz)	43.0 $\mu\text{s}$ (23.3 kHz)
$C_3 = 56 \text{ pF}$ $C_4 = 220 \text{ pF}$	89.6 $\mu\text{s}$ (11.2 kHz)	92.0 $\mu\text{s}$ (10.9 kHz)
$C_3 = 100 \text{ pF}$ $C_4 = 47 \text{ pF}$	31.0 $\mu\text{s}$ (32.3 kHz)	33.0 $\mu\text{s}$ (30.3 kHz)
$C_3 = 100 \text{ pF}$ $C_4 = 220 \text{ pF}$	67.0 $\mu\text{s}$ (14.9 kHz)	70.0 $\mu\text{s}$ (14.3 kHz)

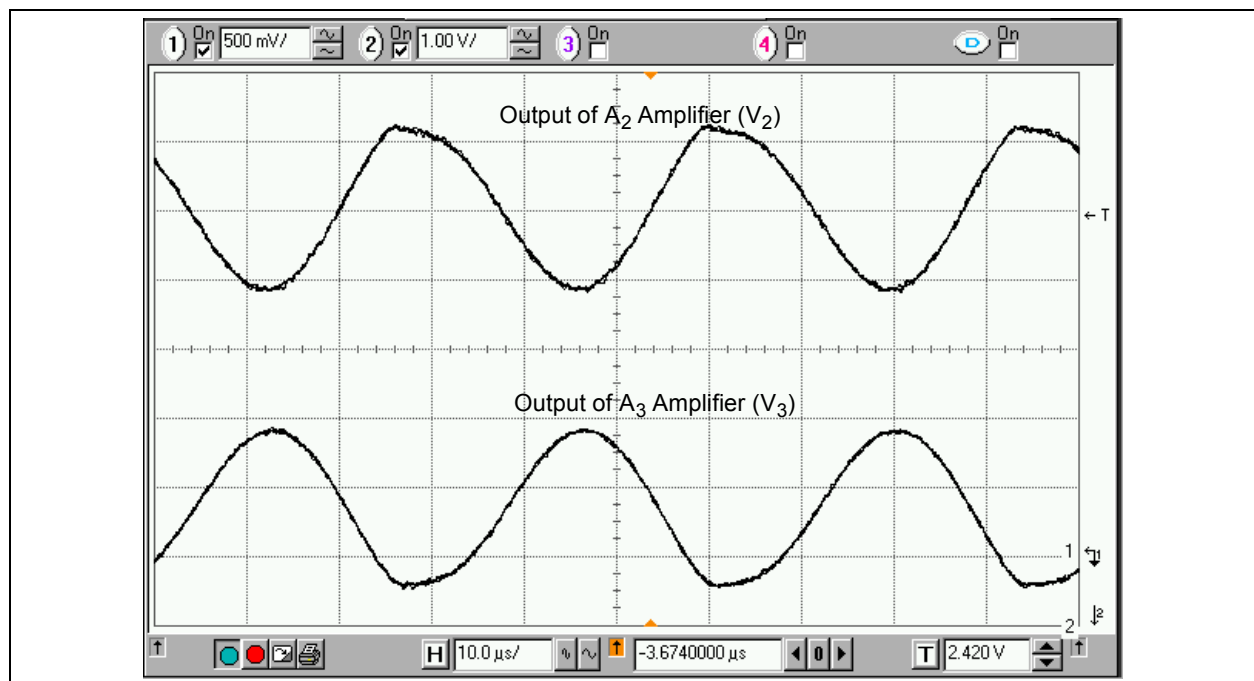

**FIGURE 9:** Ratio Oscillator Test Results ( $C_3 = 100 \text{ pF}$ ,  $C_4 = 47 \text{ pF}$ ).

## APPENDIX A: MASON'S REDUCTION THEOREM

The oscillation frequency is determined by finding the poles of the denominator of the transfer equation  $T(s)$  or equivalently the zeroes of the numerator  $N(s)$  of the characteristic equation  $\Delta(s)$ . Mason's theory is especially useful for analyzing oscillators that have multiple feedback loops.

Mason's theorem [5] states that the transfer function from input X to output Y is:

### EQUATION:

$$T(s) = \frac{Y}{X} = \frac{\sum_i P_i \Delta s_i}{\Delta s} = \frac{\sum_i P_i \Delta s_i}{\frac{N(s)}{D(s)}}$$

Where:

$P_i$  = the direct transmittance or path from input X to output Y

$\Delta s_i$  = the system determinant. ( $\Delta s_i = 1$  if  $P_i$  touches all of the loops)

$\Delta s = 1 - \sum L_j + \sum L_k L_l - \sum L_m L_n L_o + \dots$

$\sum L_j$  = the sum of all loops (i.e. loop gains)

$\sum L_k L_l$  = the sum of products of pairs of non-touching loops

$\sum L_m L_n L_o$  = the sum of products of gains of non-touching loops taken three at a time.

## APPENDIX B: ROUTH STABILITY TEST

The Routh Stability Test [5] can be used to test the characteristic equation to determine whether any of the roots lie on the imaginary axis. Routh's test consists of forming a coefficient array from  $N(s)$ . Next, the procedure substitutes  $s = j\omega_0$  for  $s$ , and the summation of the row is set to zero. If the row equation produces a non-trivial solution for  $\omega_0$ , the procedure is complete and the frequency of oscillation is equal to  $\omega_0$ . If the row equation does not yield an equation that can be solved for  $\omega_0$ , the procedure continues with the next row in the Routh array. This technique arranges the numerator of the characteristic equation (i.e., denominator of the transfer equation) into the array listed below.

### EQUATION:

$$N(s) = a_0 s^n + a_1 s^{n-1} + a_2 s^{n-2} + a_3 s^{n-3} + \dots + a_{n-1} s + a_n$$

Note for simplicity, only the first three rows of the Routh coefficient array are shown below.

$$\begin{array}{cccccc} s^n & a_0 & a_2 & a_4 \dots & a_n & \\ s^{n-1} & a_1 & a_3 & a_5 \dots & a_{n-1} & \\ s^{n-2} & b_1 & b_2 & b_3 \dots & b_{n-2} & \end{array}$$

where the coefficients  $b_1, b_2, b_3$ , etc., are defined as:

$$b_1 = (a_1 a_2 - a_0 a_3) / a_1$$

$$b_2 = (a_1 a_4 - a_0 a_5) / a_1$$

$$b_3 = (a_1 a_6 - a_0 a_7) / a_1$$

The Routh stability criterion states:

1. A necessary and sufficient condition for stability is that the first column of the array does not contain sign changes.
2. The number of sign changes in the entries of the first column of the array is equal to the number of roots in the right half  $s$ -plane.
3. If the first element in a row is zero, it is replaced by  $\epsilon$ , and the sign changes when  $\epsilon \rightarrow 0$  are counted after completing the array.
4. The poles are located in the right half plane or on the imaginary axis if all the elements in a row are zero.

## CONCLUSION

Operational amplifier oscillators can be used to produce a frequency that is proportional to resistive and capacitive sensors. Design equations defining the oscillation frequency are readily available for several common oscillators, such as Wein bridge and phase shift oscillators. However, detailed design equations that show the relationship of the resistors and capacitors are generally not available. Thus, there is a need for a design procedure that derives the equations in order to select the resistor and capacitor components that maximize the accuracy of the oscillation frequency. The design procedure was demonstrated by analyzing two state-variable oscillators for capacitive sensing applications.

## BIBLIOGRAPHY

1. Celma, C., Martinez, P., and Carlosens, A., "Approach to the Synthesis of Canonic RC-Active Oscillators Using CCI", IEE Proc. Circuits, Devices and Systems, Vol. 141, No. 6, December 1994, pp. 493-497.
2. Lepkowski, J. and Young, C., "AND8054 - Designing RC Oscillator Circuits with Low Voltage Operational Amplifiers and Comparators for Precision Sensor Applications", ON Semiconductor, Phoenix, Arizona, 2002.
3. Martinez, P., Aldea C. and Celma, S., "Approach to the Realization of State-Variable Based Oscillators", IEEE International Conference on Electronics Circuits and Systems, Vol. 3, 1998, p.139-142.
4. Sidorowicz, R., "An Abundance of Sinusoidal RC-Oscillators", Proc. IEE, Vol. 119, No. 3, March 1972, pp. 283-293.
5. Truxal, J., "Introductory System Engineering", McGraw-Hill, N.Y., 1972.
6. Van Valkenburg, M., "Analog Filter Design", Saunders College Publishing, Fort Worth, 1992.

NOTES:

---

---

**Note the following details of the code protection feature on Microchip devices:**

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

---

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

#### Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, KEELoQ, MPLAB, PIC, PICmicro, PICSTART, PRO MATE and PowerSmart are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

FilterLab, microID, MXDEV, MXLAB, PICMASTER, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Accuron, Application Maestro, dsPICDEM, dsPICDEM.net, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, PICC, PICkit, PICDEM, PICDEM.net, PowerCal, PowerInfo, PowerMate, PowerTool, rLAB, rPIC, Select Mode, SmartSensor, SmartShunt, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2003, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.



*Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999 and Mountain View, California in March 2002. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELoQ® code hopping devices, Serial EEPROMs, microperipherals, non-volatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.*



## WORLDWIDE SALES AND SERVICE

### AMERICAS

#### Corporate Office

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200 Fax: 480-792-7277  
Technical Support: 480-792-7627  
Web Address: <http://www.microchip.com>

#### Atlanta

3780 Mansell Road, Suite 130  
Alpharetta, GA 30022  
Tel: 770-640-0034 Fax: 770-640-0307

#### Boston

2 Lan Drive, Suite 120  
Westford, MA 01886  
Tel: 978-692-3848 Fax: 978-692-3821

#### Chicago

333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 630-285-0071 Fax: 630-285-0075

#### Dallas

4570 Westgrove Drive, Suite 160  
Addison, TX 75001  
Tel: 972-818-7423 Fax: 972-818-2924

#### Detroit

Tri-Atria Office Building  
32255 Northwestern Highway, Suite 190  
Farmington Hills, MI 48334  
Tel: 248-538-2250 Fax: 248-538-2260

#### Kokomo

2767 S. Albright Road  
Kokomo, IN 46902  
Tel: 765-864-8360 Fax: 765-864-8387

#### Los Angeles

18201 Von Karman, Suite 1090  
Irvine, CA 92612  
Tel: 949-263-1888 Fax: 949-263-1338

#### Phoenix

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7966 Fax: 480-792-4338

#### San Jose

Microchip Technology Inc.  
2107 North First Street, Suite 590  
San Jose, CA 95131  
Tel: 408-436-7950 Fax: 408-436-7955

#### Toronto

6285 Northam Drive, Suite 108  
Mississauga, Ontario L4V 1X5, Canada  
Tel: 905-673-0699 Fax: 905-673-6509

### ASIA/PACIFIC

#### Australia

Microchip Technology Australia Pty Ltd  
Marketing Support Division  
Suite 22, 41 Rawson Street  
Epping 2121, NSW  
Australia  
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

#### China - Beijing

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Beijing Liaison Office  
Unit 915  
Bei Hai Wan Tai Bldg.  
No. 6 Chaoyangmen Beidajie  
Beijing, 100027, No. China  
Tel: 86-10-85282100 Fax: 86-10-85282104

#### China - Chengdu

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Chengdu Liaison Office  
Rm. 2401-2402, 24th Floor,  
Ming Xing Financial Tower  
No. 88 TIDU Street  
Chengdu 610016, China  
Tel: 86-28-86766200 Fax: 86-28-86766599

#### China - Fuzhou

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Fuzhou Liaison Office  
Unit 28F, World Trade Plaza  
No. 71 Wusi Road  
Fuzhou 350001, China  
Tel: 86-591-7503506 Fax: 86-591-7503521

#### China - Hong Kong SAR

Microchip Technology Hongkong Ltd.  
Unit 901-6, Tower 2, Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T., Hong Kong  
Tel: 852-2401-1200 Fax: 852-2401-3431

#### China - Shanghai

Microchip Technology Consulting (Shanghai)  
Co., Ltd.  
Room 701, Bldg. B  
Far East International Plaza  
No. 317 Xian Xia Road  
Shanghai, 200051  
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

#### China - Shenzhen

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Shenzhen Liaison Office  
Rm. 1812, 18/F, Building A, United Plaza  
No. 5022 Binhe Road, Futian District  
Shenzhen 518033, China  
Tel: 86-755-82901380 Fax: 86-755-8295-1393

#### China - Qingdao

Rm. B505A, Fullhope Plaza,  
No. 12 Hong Kong Central Rd.  
Qingdao 266071, China  
Tel: 86-532-5027355 Fax: 86-532-5027205

#### India

Microchip Technology Inc.  
India Liaison Office  
Marketing Support Division  
Divyasree Chambers  
1 Floor, Wing A (A3/A4)  
No. 11, O'Shaughnessy Road  
Bangalore, 560 025, India  
Tel: 91-80-2290061 Fax: 91-80-2290062

### Japan

Microchip Technology Japan K.K.  
Benex S-1 6F  
3-18-20, Shinyokohama  
Kohoku-Ku, Yokohama-shi  
Kanagawa, 222-0033, Japan  
Tel: 81-45-471-6166 Fax: 81-45-471-6122

### Korea

Microchip Technology Korea  
168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku  
Seoul, Korea 135-882  
Tel: 82-2-554-7200 Fax: 82-2-558-5934

### Singapore

Microchip Technology Singapore Pte Ltd.  
200 Middle Road  
#07-02 Prime Centre  
Singapore, 188980  
Tel: 65-6334-8870 Fax: 65-6334-8850

### Taiwan

Microchip Technology (Barbados) Inc.,  
Taiwan Branch  
11F-3, No. 207  
Tung Hua North Road  
Taipei, 105, Taiwan  
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

### EUROPE

#### Austria

Microchip Technology Austria GmbH  
Durisolstrasse 2  
A-4600 Wels  
Austria  
Tel: 43-7242-2244-399  
Fax: 43-7242-2244-393

#### Denmark

Microchip Technology Nordic ApS  
Regus Business Centre  
Lautrup høj 1-3  
Ballerup DK-2750 Denmark  
Tel: 45-4420-9895 Fax: 45-4420-9910

#### France

Microchip Technology SARL  
Parc d'Activite du Moulin de Massy  
43 Rue du Saule Trapu  
Batiment A - ler Etage  
91300 Massy, France  
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

#### Germany

Microchip Technology GmbH  
Steinheilstrasse 10  
D-85737 Ismaning, Germany  
Tel: 49-89-627-144-0  
Fax: 49-89-627-144-44

#### Italy

Microchip Technology SRL  
Via Quasimodo, 12  
20025 Legnano (MI)  
Milan, Italy  
Tel: 39-0331-742611 Fax: 39-0331-466781

#### United Kingdom

Microchip Ltd.  
505 Eskdale Road  
Winkersham Triangle  
Wokingham  
Berkshire, England RG41 5TU  
Tel: 44-118-921-5869 Fax: 44-118-921-5820

05/30/03