

# Multistage Amplifiers

- Single-stage transistor amplifiers are inadequate for meeting most design requirements for **any** of the four amplifier types (voltage, current, transconductance, and transresistance.)
- Therefore, we use more than one amplifying stage. The challenge is to gain insight into when to use which of the **12** single stages that are available in a modern BiCMOS process:

*Bipolar Junction Transistor:* CE, CB, CC -- in npn and pnp\* versions

*MOSFET:* CS, CG, CD -- in n-channel and p-channel versions

\* in many BiCMOS technologies, only the npn BJT is available

- How to design multi-stage amplifiers that satisfy the required performance goals?

## \* Two fundamental requirements:

### 1. Impedance matching:

output resistance of stage  $n$ ,  $R_{out, n}$  and input resistance of stage  $n + 1$ ,  $R_{in, (n+1)}$ , must be in the proper ratio

$$R_{in, (n+1)} / R_{out, n} \rightarrow \infty \quad \text{or} \quad R_{in, (n+1)} / R_{out, n} \rightarrow 0$$

to avoid degrading the overall gain parameter for the amplifier


### 2. DC coupling:

direct connection between stages --> interaction between biasing sources must be considered (later)
 
## Cascaded Voltage Amplifier

- Want  $R_{in} \rightarrow \infty$ ,  $R_{out} \rightarrow 0$ , with high voltage gain.


Try CS as first stage, followed by CS to get more gain ... use 2-port models



- solve for overall voltage gain ... higher, but  $R_{out} = R_{out2}$  which is too large
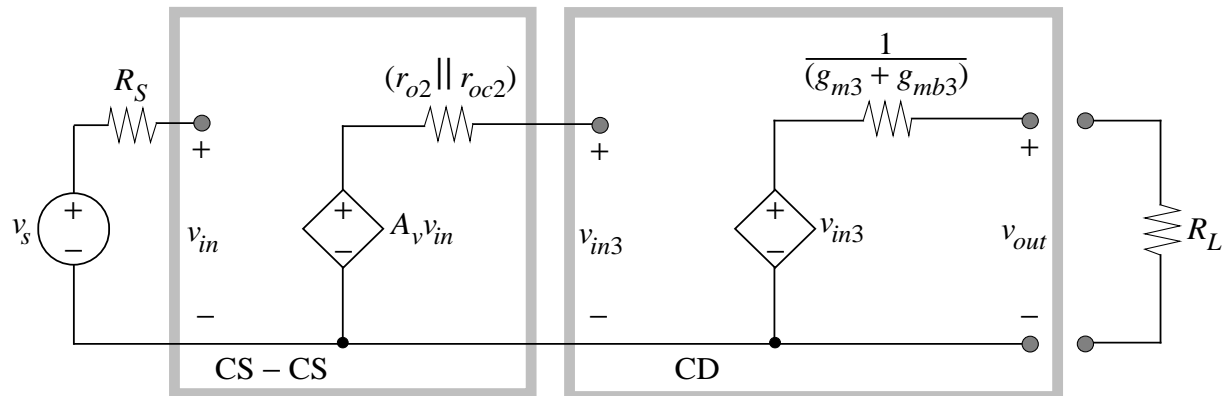
## Three-Stage Voltage Amplifier


- Fix output resistance problem by adding a common drain stage (voltage buffer)



- Output resistance is not that low ... few  $k\Omega$  for a typical MOSFET and bias --> could pay an area penalty by making  $(W/L)$  very large to fix.
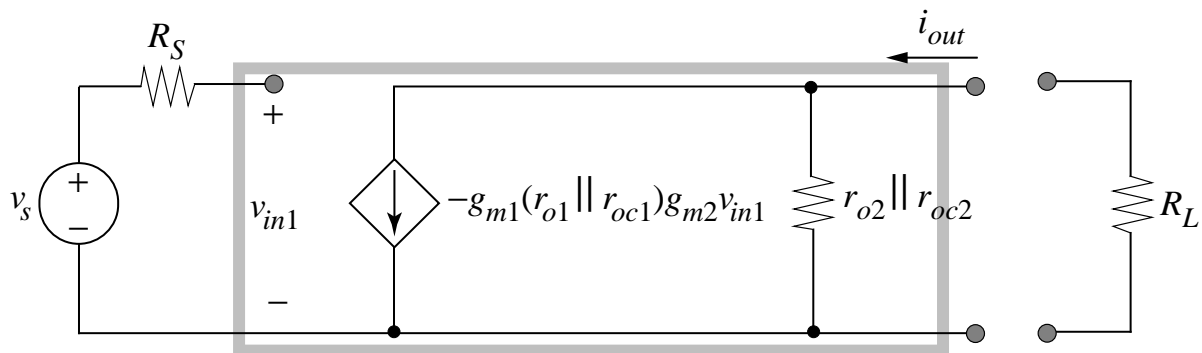
## Transconductance Amplifier


- input resistance should be high; output resistance should also be high
- initial idea: use CS stages (they are “natural” transconductance amps)



- Overall  $G_m = -g_{m1}(r_{o1} \parallel r_{oc1})g_{m2} = A_{v1}g_{m2} \dots$  can be very large
- Output resistance is only moderately large
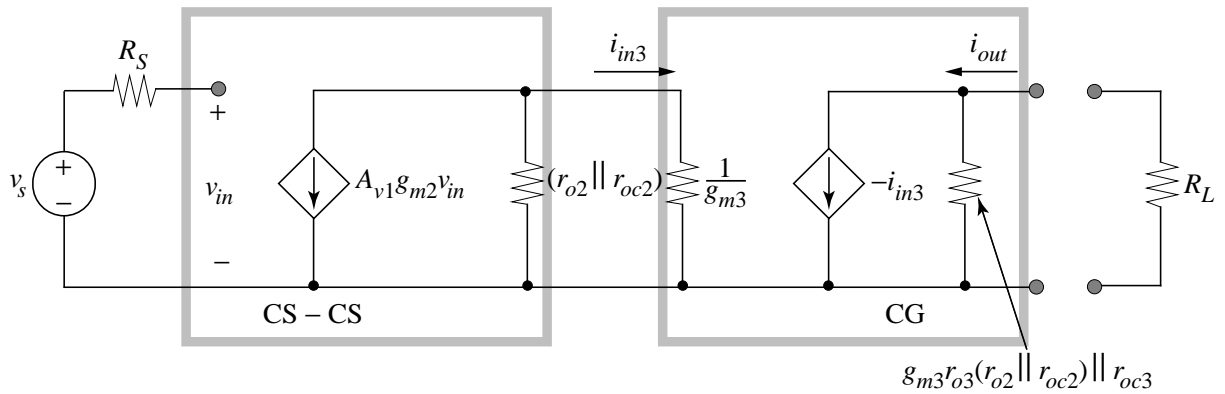
# Improved Transconductance Amplifier


- Output resistance: boost using CB or CG stage



- high-resistance current sources are needed to avoid having  $r_{oc3}$  limit the resistance
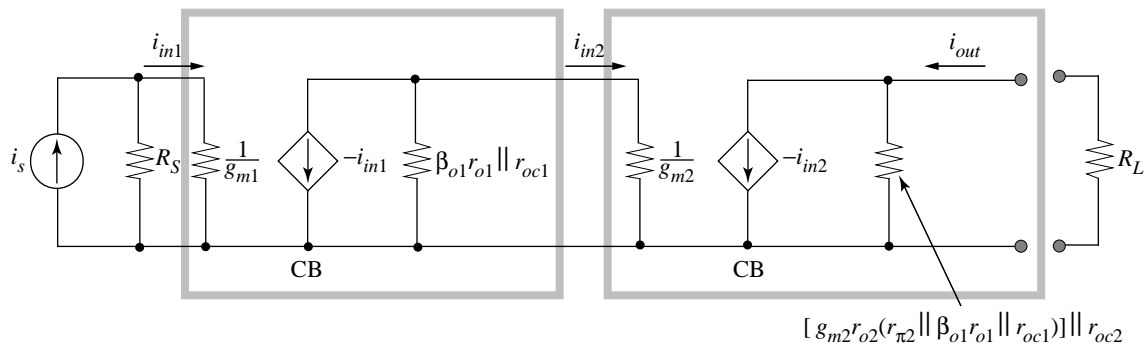
## Two-Stage Current Buffers

- since one CB stage boosted the output resistance substantially, why not add another one ...



- The base-emitter resistance of the 2<sup>nd</sup> stage BJT is  $r_{\pi2}$  which is much less than the 2<sup>nd</sup> stage source resistance = 1<sup>st</sup> stage output resistance

$$R_{S2} = R_{out1} = \beta_{o1}r_{o1} \parallel r_{oc1}$$


- Therefore, the output resistance expression reduces to

$$R_{out} \approx g_{m2}r_{o2}r_{\pi2} \parallel r_{oc2} = \beta_{o2}r_{o2} \parallel r_{oc2}$$

... no improvement over a single CB stage
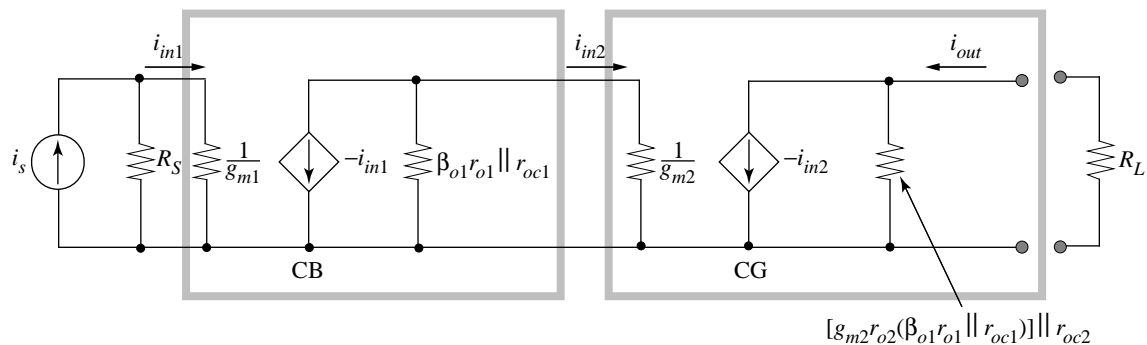
## Improved Current Buffer: CB/CG

- The addition of a common-gate stage results in further increases in the output resistance, making the current buffer closer to an ideal current source at the output port



- The product of transconductance and output resistance  $g_{m2} r_{o2}$  can be on the order of 500 - 900 for a MOSFET -->  $R_{out}$  is increased by over two orders of magnitude

Of course, the current supply for the CG stage has to have at least the same order of output resistance in order for it not to limit the overall  $R_{out}$ .

Practical limit ... on the order of  $100\text{ M}\Omega$

## DC Coupling: General Trends

- **Goal:** want both input and output to be “centered” at halfway between the positive and negative supplies (or ground, for a single supply) -- in order to have maximum possible swing at the input and at the output.

Summary of DC shifts through the single stages:

BJT Amp. Type	nnp version	pnp version
CE	positive	negative
CB	positive	negative
CC	negative*	positive*


MOS Amp. Type	n-channel version	p-channel version
CS	positive	negative
CG	positive	negative
CD	negative*	positive*

The DC voltage shifts for CC/CD stages are set by the  $V_{BE} = 0.7\text{ V}$  drop or by the  $V_{GS}$  of the transistor and can be specified by the designer.


 
## DC Coupling Example

- Common drain - common collector cascade (infinite input resistance, fairly low output resistance, unity voltage gain ... reasonable voltage buffer)



For CC stage, the optimum output voltage of 2.5 V (centered between + 5 V and ground for maximum swing) -->

$$V_{IN2} = \text{DC input of CC amp} = 2.5 + 0.7 \text{ V} = 3.2 \text{ V}$$

The DC of the n-channel CD amplifier is then:


$$V_{IN} = \text{DC input of CD amp} = V_{IN2} + V_{GS1} = 3.2 \text{ V} + 1.5 \text{ V} = 4.7 \text{ V}$$

where we have assumed that  $V_{GS1} = 1.5 \text{ V}$  as a typical gate-source voltage (actual number comes from  $I_{SUP1}$  and  $(W/L)$ ).

- too close to the supply voltage -- input DC level should be centered at near 2.5 V.
 
## DC Biasing Example (Cont.)


- Solution: use p-channel CD amplifier since it shifts the DC level in the **positive** direction from input to output



Selection of large ( $W/L$ ) for the p-channel --> input DC level can be adjusted closer to 2.5 V.

## Sharing a Current Supply: Current Buffer

 
- Example: CB/CG cascade that shares common supply and bias sources


 
## Sharing a Current Supply: the Cascode

- Common-source/common-base two-stage amplifier:

common-source transistor is used to provide bias current to the common-base transistor




- Similar configurations are also referred to as a “cascode topology:  
CE/CB, CE/CG, CS/CB, and CS/CG are also cascodes

## DC Voltage and Current Sources

- Output characteristic of a BJT or MOSFET look like a family of current sources ... how do we pick one?

specify the gate-source *voltage*  $V_{GS}$  in order to select the desired current level for a MOSFET ( specify  $V_{BE}$  for a BJT)

 how do we generate a precise voltage? ... we use a current source to set the current in a “diode-connected” MOSFET



(wait a minute ... where do we find  $I_{REF}$ ? Assume that one is available)

$$i_D = I_{REF} + i_{OUT} = \left(\frac{W}{2L}\right)\mu_n C_{ox}(v_{OUT} - V_{Tn})^2$$

(neglect channel-length modulation term)

## DC Voltage Sources (cont.)

- Solving for the output voltage

$$v_{OUT} = V_{Tn} + \sqrt{\frac{I_{REF} + i_{OUT}}{\left(\frac{W}{2L}\right)\mu_n C_{ox}}}$$


If  $I_D = 100 \mu\text{A}$ ,  $\mu_n = 50 \mu\text{AV}^{-2}$ ,  $(W/L) = 20$ ,  $V_{Tn} = 1 \text{ V}$ , then

$$V_{OUT} = 1.45 \text{ V for } I_{OUT} = 0 \text{ A.}$$

- bias current and MOSFET dimensions set the  $I_{OUT}$  vs.  $V_{OUT}$  characteristic
 
## Source Resistance of Voltage Source

- Small-signal model of MOSFET with drain shorted to gate (“diode-connected”)



transconductance generator degenerates into a conductance  
(since  $v_{gs}$  is now the voltage drop across it)

- Source resistance of voltage source (assume  $I_{REF}$  has  $r_{oc} \rightarrow \infty$ )

$$R_S = \frac{v_t}{i_t} = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

## Voltage Source Equivalent Circuit (Around $I_{OUT} = 0$ A)

- Similar to idealized current source equivalent circuit
- Place incremental resistance  $1/g_m$  in series with value of voltage source with  $I_{OUT} = 0$  A

