

# LM359

*Application Brief 24 Bench Testing LM3900 and LM359 Input Parameters*



Literature Number: SNOA588

# Bench Testing LM3900 and LM359 Input Parameters

National Semiconductor  
 Application Brief 24  
 September 1985



Two input parameters are extremely important in designing circuits with Norton op amps. These are the input bias current,  $I_{BIAS}$ , and the mirror gain constant,  $A_I$ . The mirror gain is especially important when a Norton amplifier is used as a voltage follower.

A simplified schematic of the LM3900 is shown in *Figure 1*. The op amp is basically a common emitter amplifier (Q3), with an emitter follower output stage. Added to the base of Q3 is a current mirror (Q1 and Q2). If a fixed current is injected into the non-inverting input and the output is fed back to the inverting input, the output will rise until the current in Q2 matches that flowing in Q1. The currents in the input terminals will not be equal since some current ( $I_{BIAS}$ ) flows into the base of Q3. This is especially noticeable when the mirror current is very small—for instance in the 1 to 10  $\mu A$  range. Input currents may also be unequal due to mismatch in the mirror transistors, Q1 and Q2. The degree of matching is called mirror gain,  $A_I$ , and is ideally equal to "1".

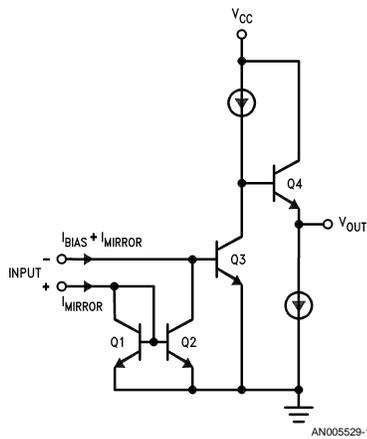


FIGURE 1. A simplified schematic of the LM3900

The LM359 (*Figure 2*) differs from the LM3900 in that "Q3" is a cascode stage, and "Q4" is a darlington follower. Also, the internal biasing is variable; set current ( $I_{SET}$ ) is determined by an external resistor. Gain-bandwidth product, slew rate, input noise, output drive current, input bias current and, of course, supply current all vary with set current.

Any modern text detailing the operation of an op amp will tell you how to bench test its parameters. Norton amplifiers are, however, frequently overlooked and their important input parameters are difficult to test in the usual manner. Two measurements and a simple calculation can provide accurate characterization of  $I_{BIAS}$  and  $A_I$ .

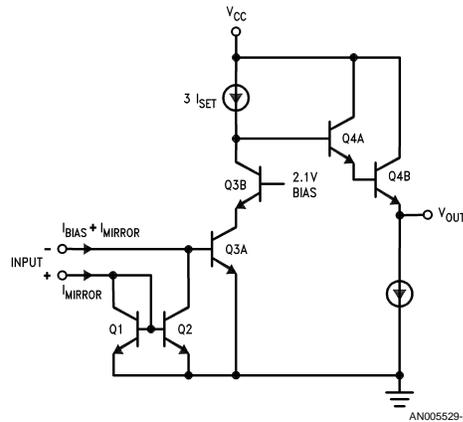


FIGURE 2. A simplified schematic of the LM359

The test circuit for measurement of  $I_{BIAS}$  in the LM3900 is shown in *Figure 3*. Two voltage measurements are made at the output of the LM3900, one with S1 closed and one with S1 opened. The output voltage increase is equal to the voltage appearing across the 1  $M\Omega$  resistor, multiplied by the closed loop gain ( $A_V$ ) of 5. It is the result of Q3 bias current flowing in the 1  $M\Omega$  resistor. For the circuit shown the output voltage increase multiplied by 200 gives the bias current in nanoamperes.

$$I_{BIAS} \text{ (nA)} = 200 \Delta V_{OUT} = \left( \frac{10^9}{A_V \times 1 \text{ M}\Omega} \right) \Delta V_{OUT}$$


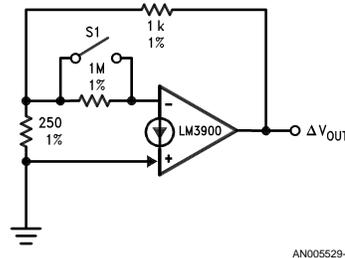


FIGURE 3.  $I_{BIAS}$  can be evaluated by measuring the change in output voltage when S1 is opened and closed.

LM3900 mirror gain is measured using the circuit of *Figure 4*. "R" is selected to provide the desired mirror current. The voltage across each "R" is measured, and their ratio is equal to the mirror gain,  $A_I$ . As previously mentioned, the mirror gain is affected by the presence of  $I_{BIAS}$ . Where  $I_{BIAS}$  is a significant part of the mirror current, the formula (true for the LM3900 and the LM359) for  $A_I$  becomes

$$A_I = \frac{(V_2) - RI_{BIAS}}{V_1}$$

Many of the LM359's data sheet parameters, including  $I_{BIAS}$ , are measured with  $I_{SET}=0.5$  mA. Three times this current flows in the collector of Q3A, making its bias current about 15  $\mu$ A. The LM3900 has a corresponding Q3 collector current of only 3  $\mu$ A, and its  $I_{BIAS}=30$  nA. However, the LM3900 doesn't have a 400 MHz gain-bandwidth product.

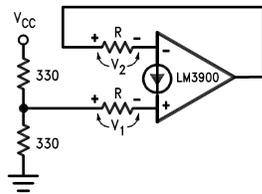


AN005529-4

$$A_I = \frac{V_2}{V_1}$$

R (1%)	$I_{MIRROR}$
270 k $\Omega$	20 $\mu$ A
27 k $\Omega$	200 $\mu$ A

**FIGURE 4.** This circuit allows the measurement of the mirror gain, " $A_I$ "

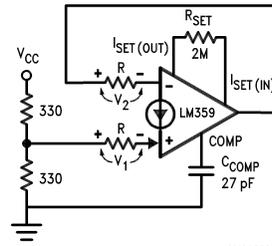

AN005529-5


$$10 \Delta V_{OUT} = I_{BIAS} (\mu A)$$

**FIGURE 5.**  $I_{BIAS}$  is measured with a set current of 500  $\mu$ A

The mirror gain is measured with  $I_{SET}=5$   $\mu$ A, making  $I_{BIAS}$  so small it has little affect on the measurement. In a practical application  $I_{BIAS}$  may be a significant part of the mirror current, adding an unpredictable error term to the DC biasing equations. This circumstance can be avoided by sizing the mirror current at least  $1/3 I_{SET}$ .

*Figures 5, 6* show how to measure and calculate  $I_{BIAS}$  and  $A_I$  for the LM359.  $R_{SET}$  is selected to provide the appropriate set current and  $C_{COMP}$  is added for stability.  $I_{BIAS}$  and  $A_I$  are measured with the same set currents used in the data sheet.

All of the test circuits assume  $V_{CC}=12$ V. Accuracy is as good as the resistors and meter used. Matching is important for the two "R"s used in *Figures 4, 6*. 1% tolerance is recommended for each resistor (5% resistors can be sorted for accuracy) in *Figure 3*, and the 100 k $\Omega$  resistor in *Figure 5*. Most 3 $\frac{1}{2}$  digit DVM's have sufficient accuracy for the voltage measurements; input impedance must be at least 10 M $\Omega$  to prevent circuit loading in the mirror gain tests. Detailed information concerning the use of the LM3900 and LM359 can be found in their data sheets and in AN-72.

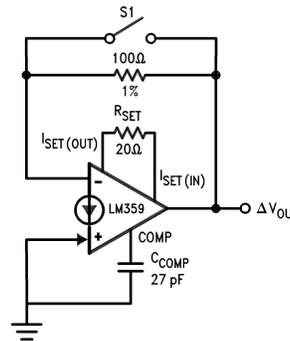


AN005529-6

$$A_I = \frac{V^-}{V^+}$$

R (1%)	$I_{MIRROR}$
270 k $\Omega$	20 $\mu$ A
27 k $\Omega$	200 $\mu$ A
2.7 k $\Omega$	2 mA

**FIGURE 6.** Mirror gain,  $A_I$ , is measured with  $I_{SET} = 5$   $\mu$ A

 

**LIFE SUPPORT POLICY**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

 <p><b>National Semiconductor Corporation</b> Americas Tel: 1-800-272-9959 Fax: 1-800-737-7018 Email: support@nsc.com</p>	<p><b>National Semiconductor Europe</b> Fax: +49 (0) 1 80-530 85 86 Email: europe.support@nsc.com Deutsch Tel: +49 (0) 1 80-530 85 85 English Tel: +49 (0) 1 80-532 78 32 Français Tel: +49 (0) 1 80-532 93 58 Italiano Tel: +49 (0) 1 80-534 16 80</p>	<p><b>National Semiconductor Asia Pacific Customer Response Group</b> Tel: 65-2544466 Fax: 65-2504466 Email: sea.support@nsc.com</p>	<p><b>National Semiconductor Japan Ltd.</b> Tel: 81-3-5620-6175 Fax: 81-3-5620-6179</p>
<p><a href="http://www.national.com">www.national.com</a></p>			

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated