
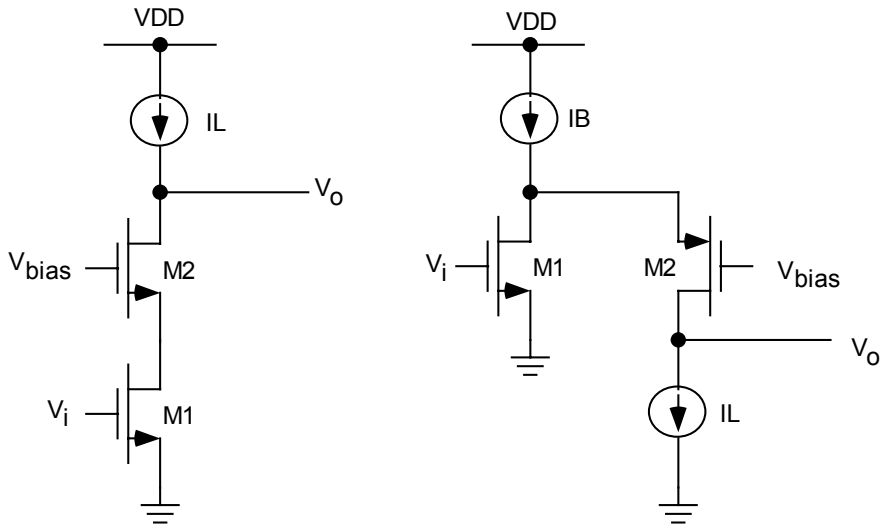


1.0 Folded-Cascode OTA

 


(a) Telescopic Cascode


(b) Folded Cascode



 
(c) Equivalent Circuit of Telescopic Cascode



(d) Equivalent Circuit of Folded Cascode

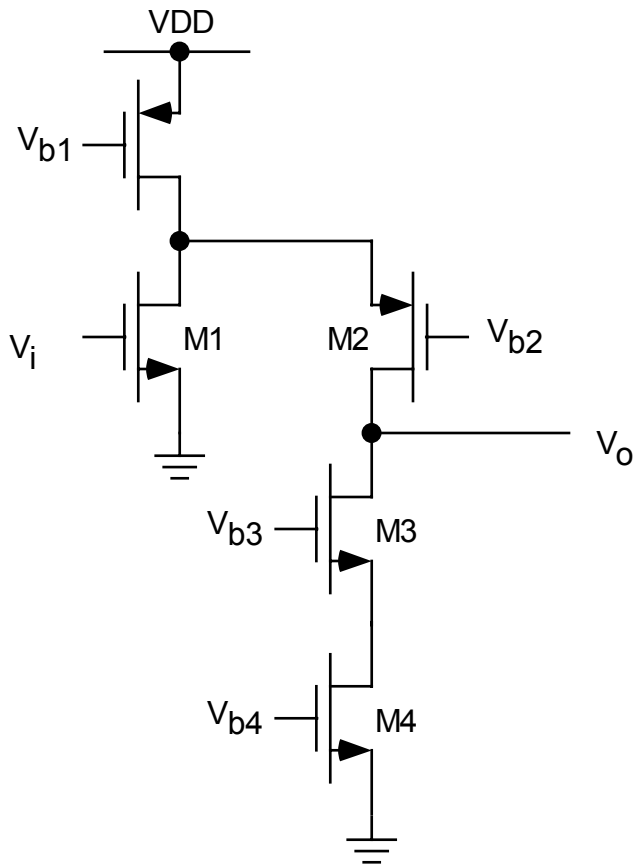

Folded Cascode With Cascode Load

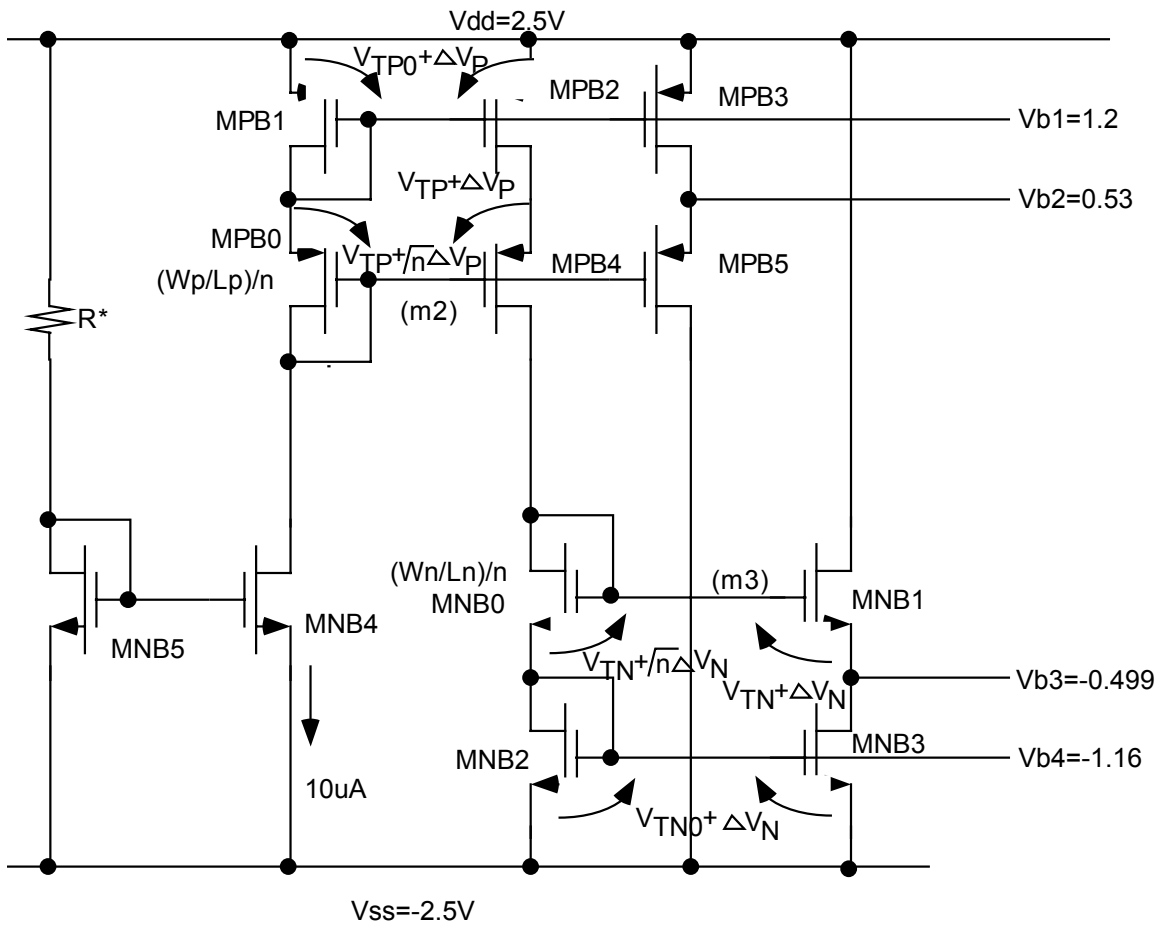

$R^*=380k$ (external resistor, adjusted to achieve the desired bias voltages as shown)

$(Wn/Ln)=(18L/6L)$
 $(Wn/Ln)/7=(6L/14L)$
 $(Wp/Lp)=(54L/6L)$
 $(Wp/Lp)/7=(9L/7L)$

Where the divisor $n=7$


```

MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vb2 PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vb1 PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss {IB}

```

* Wide Swing OTA Implementation

```

MN1 n1 in+ n3 vss NMOS1 W={Wn} L={Ln}
MN2 n2 in- n3 vss NMOS1 W={Wn} L={Ln}
MN3 n3 vb3 n7 vss NMOS1 W={Wn} L={Ln}
MN4 n7 vb4 vss vss NMOS1 W={Wn} L={Ln}
MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 out vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 out vb2 n2 vdd PMOS1 W={Wp} L={Lp}
.ENDS

```

```

.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9


```


* Analysis

```

.DC Vin -3.5V 3.5V .05V
.PROBE
.END

```

 

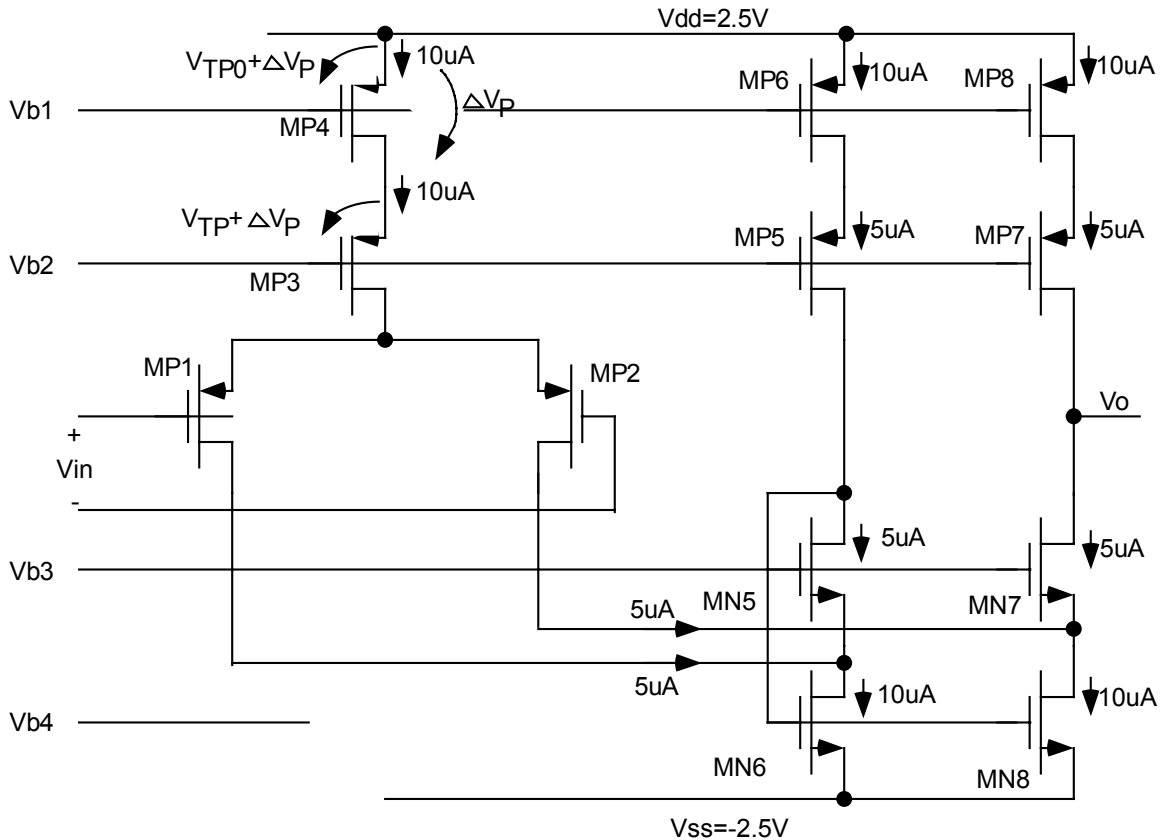

*NOTE: All transistors are 3-terminal type (D,G,S) with
 NMOS bulk (B) connected to VSS, and (Wn/Ln)=(18L/6L)
 PMOS bulk (B) connected to VDD (Wp/Lp)=(54L/6L)

* Filename="wsotadc2.cir"
 * Wide-swing OTA
 * Simulation using subckt
 * PMOS input stage=>poor positive input CMR
 * OTA inputs
 Vin 1 0 DC 0V

Xwsota 1 3 3 WSOTA
 *Xwsota 1 0 3 WSOTA
 *VS 3 0 DC 0V

.SUBCKT WSOTA in+ in- out
 * Power supplies
 VDD vdd 0 DC 2.5V
 VSS vss 0 DC -2.5V

* Wmin=Lmin=6 Lambda for linear analog circuit
 .PARAM Wn=10.8U, Ln=3.6U
 .PARAM Wp=32.4U, Lp=3.6U
 .PARAM Wn7=3.6U, Ln7=8.4U
 .PARAM Wp7=5.4U, Lp7=4.2U
 .PARAM IB=10UA

```

* Biasing Circuit to generates vb1, vb2, vb3, vb4
MPB1 vb1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vb2 PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vb1 PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss {IB}

```

* Wide Swing OTA Implementation

```

MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 out vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 out vb2 n2 vdd PMOS1 W={Wp} L={Lp}
MP1 n5 in+ n8 vdd PMOS1 W={Wp} L={Lp}
MP2 n6 in- n8 vdd PMOS1 W={Wp} L={Lp}
MP4 n9 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP3 n8 vb2 n9 vdd PMOS1 W={Wp} L={Lp}
.ENDS

```

```

.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9


```

* Analysis

```

.DC Vin -3.5V 3.5V .05V
.PROBE
.END

```

 2.0 Wide-Swing Folded-Cascode OTA

The problem with differential amplifier with nmos input pair is that the positive CMR extends beyond VDD, while the negative CMR is limited by the minimum voltage across the differential input. On the other hand the problem with differential amplifier with pmos input pair is that the positive CMR is limited by the minimum voltage across the differential input, while the negative CMR extend beyond VSS. Figure 2 shows a wide-swing differential amplifier which extends the input CMR beyond the power supply rails by combining both the nmos and pmos input pairs differential amplifiers. The circuit utilized folded-cascode load to increase the output impedance to approach ∞ , the output impedance of ideal OTA. To increase the output impedance, $(W/L)_n=3$ and $(W/L)_p=3*(W/L)_n=9$ are chosen. To reduce the effect of length modulation $(2*DL)=1\mu$, the minimum length $L=6\mu$ is chosen. Figure 1 shows the biasing circuit which generates the four biasing voltages for the wide-swing folded-cascode OTA. This biasing circuit has been discuss earlier. In the ideal case of ignoring the bulk effects, the ratio needed to achieve the desired biasing voltages is $1/4$. But with the bulk effects included this ratio needs to be adjusted to guarantee that a ¹10uA current flows in MP3, MP4, MN3, MN4. Experimentation with the given circuit, the best ratio was found to be $1/7$. The circuit was simulated to determine its specification:

$$A_v=93,560$$

$$R_o=1.095G$$

$$G_m= A_v/R_o=85.44\mu$$

This transconductance value of 85.44μ was used in all the examples, so that the response of both the ideal OTA and actual OTA implementations can be compared. The wide-swing characteristic is simulated by applying input ranging from $-3.5v$ to $3.5v$ with a power rails of $-2.5v$ and $2.5v$.The wide swing characteristic is important when designing filter circuit with high Q in cascaded filter implementation,

¹ Filename=wsota.doc

where the output of one stage is the input of the next stage. The high Q stage could easily drive the output voltage beyond the power rails.


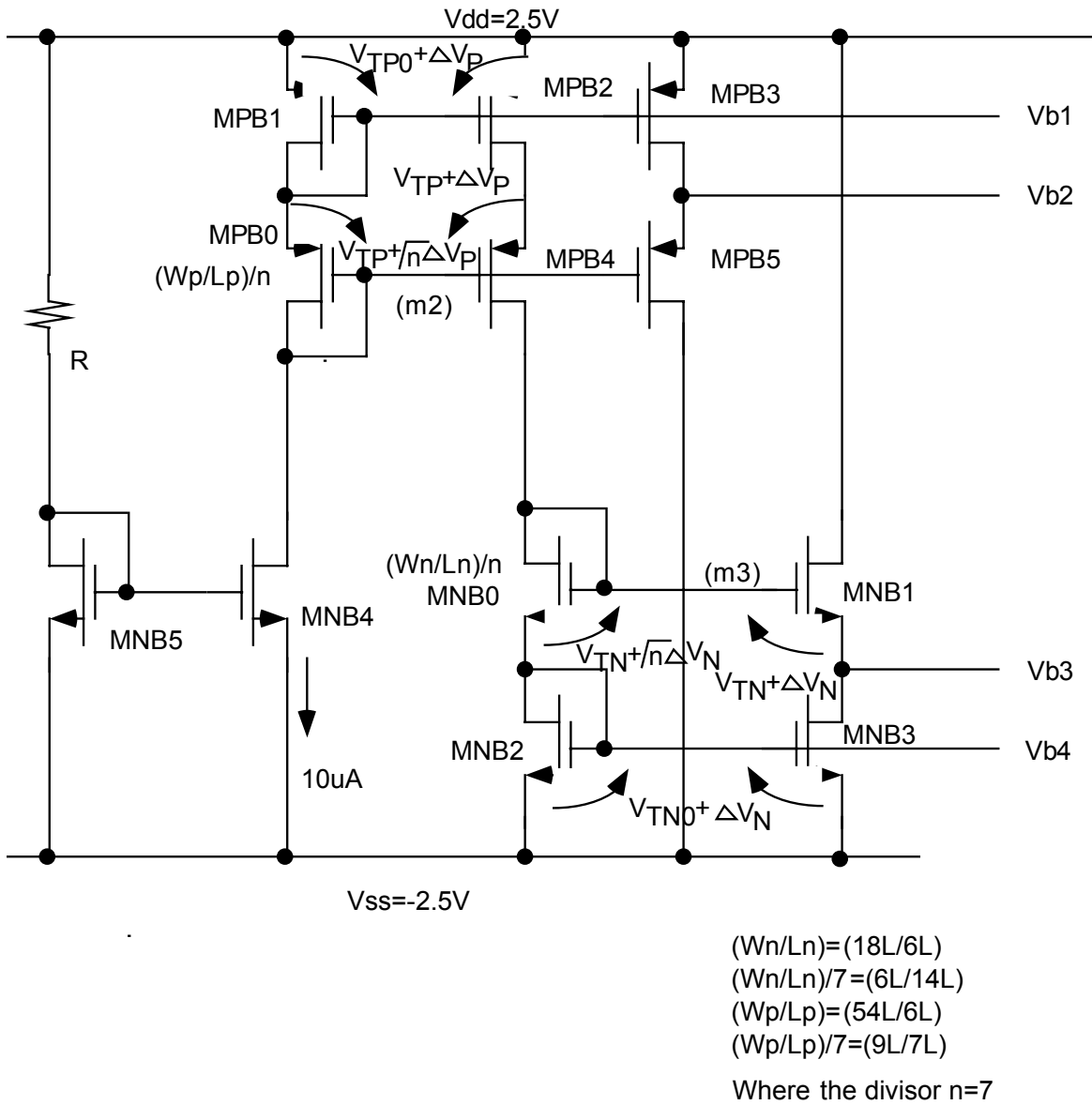


Figure 1. Biasing circuit for the wide-swing folded-cascode OTA.

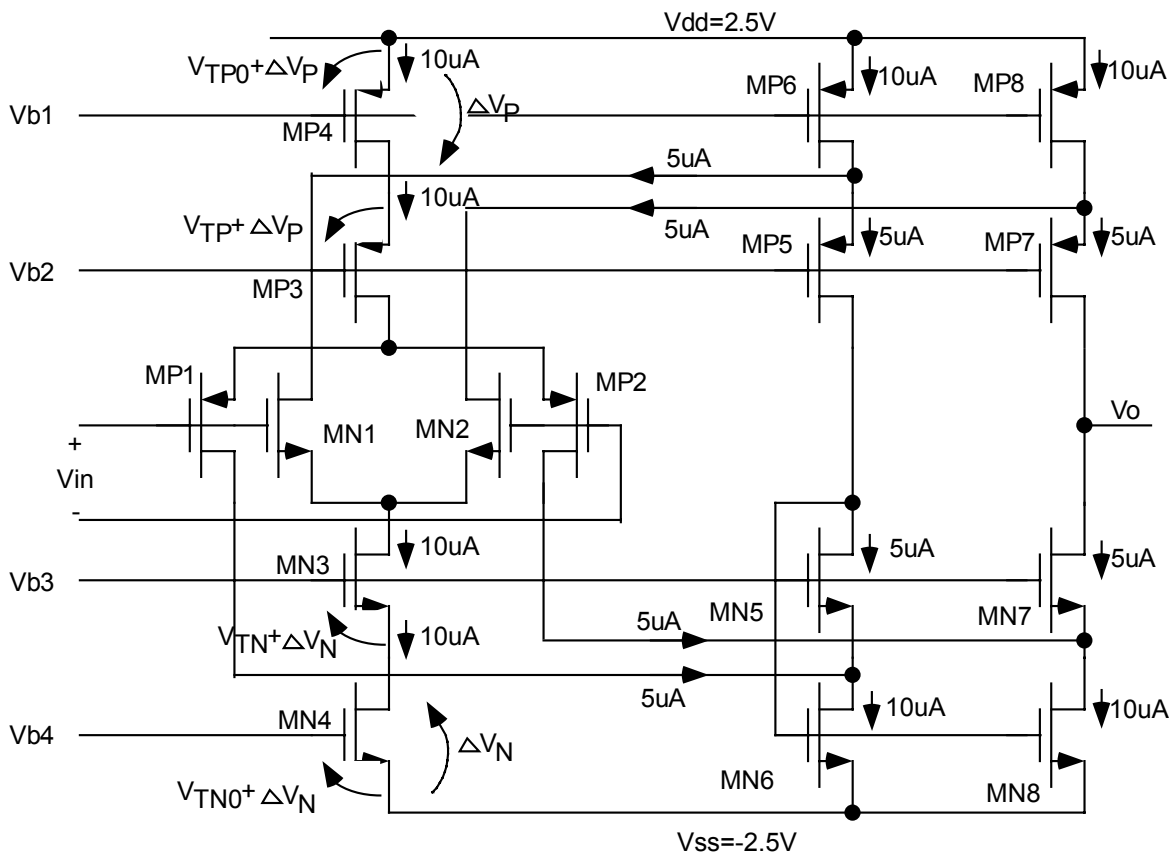

*NOTE: All transistors are 3-terminal type (D,G,S) with
 NMOS bulk (B) connected to VSS, and
 PMOS bulk (B) connected to VDD

$(W_n/L_n)=(18L/6L)$
 $(W_p/L_p)=(54L/6L)$

Figure 2. Wide-swing folded-cascode OTA

Wide Swing Single Ended OTA Circuit

Wide Swing OTA Netlist

```
* Filename ="wsotatf.cir"
* Wide-swing OTA
* Simulation showing all components
* Wmin=Lmin=6 Lambda for linear analog circuit
.PARAM Wn=10.8U, Ln=3.6U
.PARAM Wp=32.4U, Lp=3.6U
.PARAM Wn7=3.6U, Ln7=8.4U
.PARAM Wp7=5.4U, Lp7=4.2U

* Power supplies
VDD vdd 0 DC 2.5V
VSS vss 0 DC -2.5V
* OTA inputs
Vin in+ 0 DC 0V AC 1V
Vb in- 0 DC 0V

* Biasing Circuit to generates vb1, vb2, vb3, vb4
MPB1 vb1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vdd PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vdd PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss 10uA


* Wide Swing OTA Implementation
MN1 n1 in+ n3 vss NMOS1 W={Wn} L={Ln}
MN2 n2 in- n3 vss NMOS1 W={Wn} L={Ln}
MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 3 vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MN3 n3 vb3 n7 vss NMOS1 W={Wn} L={Ln}
MN4 n7 vb4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 3 vb2 n2 vdd PMOS1 W={Wp} L={Lp}
MP1 n5 in+ n8 vdd PMOS1 W={Wp} L={Lp}
MP2 n6 in- n8 vdd PMOS1 W={Wp} L={Lp}
MP4 n9 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP3 n8 vb2 n9 vdd PMOS1 W={Wp} L={Lp}

.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9

* Analysis
.AC DEC 10 1Hz 100MegHz
.TF V(3) Vin
```

```
.PROBE
.OP
.END
```

OTA Frequency Response

 

Theoretical gain calculation of the OTA

At the operating point, the biasing currents are shown in Figure 12.

$$\lambda = \lambda_N = \lambda_P = 0.02$$

$$r_{DS}(P7) = r_{DS}(N7) = \frac{1}{\lambda I_{DSQ7}} = \frac{1}{(0.02)(5E-6)} = 10E6$$

$$r_{DS}(P8) = r_{DS}(N8) = \frac{1}{\lambda I_{DSQ8}} = \frac{1}{(0.02)(10E-6)} = 5E6$$

$$g_m(N1) = g_m(N7) = \sqrt{2\beta_N I_{DSQ}} = \sqrt{2K_N (W_n/L_n) I_{DSQ}} = \sqrt{2(40E-6)(10.6/(3.6-1))(5E-6)} = 40.38E-6$$

$$g_m(P1) = g_m(P7) = \sqrt{2\beta_P I_{DSQ}} = \sqrt{2K_P (W_p/L_p) I_{DSQ}} = \sqrt{2(15E-6)(32.4/(3.6-1))(5E-6)} = 43.23E-6$$

$$R_{ON} = g_m(N7)r_{DS}(N7)r_{DS}(N8) = (37.947E-6)(10E6)(5E6) = 1.8935E9$$

$$R_{OP} = g_m(P7)r_{DS}(P7)r_{DS}(P8) = (40.249E-6)(10E6)(5E6) = 2.01245E9$$

$$R_O = R_{ON} // R_{OP} = \frac{R_{ON} R_{OP}}{R_{ON} + R_{OP}} = \frac{(1.8935E9)(2.01245E9)}{(1.8935E9) + (2.01245E9)} = 1.19E9$$

$$g_m = g_m(N1) + g_m(P1) = (40.38E-6) + (43.23E-6) = 83.61E-6$$

$$A_V = -g_m R_O = -(83.61E-6)(1.19E9) = -9.9E4$$

The OTA is simulated, the results shown below are very closed to the calculated one.

**** SMALL-SIGNAL CHARACTERISTICS

V(3)/Vin = 9.356E+04

INPUT RESISTANCE AT Vin = 1.000E+20

OUTPUT RESISTANCE AT V(3) = 1.095E+09

$$g_m = \frac{A_v}{R_o} = \frac{9.356E4}{1.095E9} = 85.44\mu$$

OTA Transfer Characteristic

* Filename="wsotadc.cir"
* Wide-swing OTA
* Simulation using subckt

* OTA inputs
Vin 1 0 DC 0V

Xwsota 1 3 3 WSOTA

.SUBCKT WSOTA in+ in- out
* Power supplies
VDD vdd 0 DC 2.5V
VSS vss 0 DC -2.5V

* Wmin=Lmin=6 Lambda for linear analog circuit
.PARAM Wn=10.8U, Ln=3.6U
.PARAM Wp=32.4U, Lp=3.6U
.PARAM Wn7=3.6U, Ln7=8.4U
.PARAM Wp7=5.4U, Lp7=4.2U
.PARAM IB=10UA

* Biasing Circuit to generates vb1, vb2, vb3, vb4
MPB1 vb1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vb2 PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vb1 PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss {IB}

* Wide Swing OTA Implementation
MN1 n1 in+ n3 vss NMOS1 W={Wn} L={Ln}
MN2 n2 in- n3 vss NMOS1 W={Wn} L={Ln}
MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 out vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MN3 n3 vb3 n7 vss NMOS1 W={Wn} L={Ln}
MN4 n7 vb4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 out vb2 n2 vdd PMOS1 W={Wp} L={Lp}
MP1 n5 in+ n8 vdd PMOS1 W={Wp} L={Lp}


```

MP2 n6 in- n8 vdd PMOS1 W={Wp} L={Lp}
MP4 n9 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP3 n8 vb2 n9 vdd PMOS1 W={Wp} L={Lp}
.ENDS

.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9

* Analysis
.DC Vin -3.5V 3.5V .05V
.PROBE
.END

```

 

Biasing The OTA Circuit

The goal of the biasing circuit shown in Figure 11 is to generate the biasing voltages needed by the OTA circuit shown in Figure 12 so that the gate to source voltages of the four transistors MN3, MN4, MP3, MP4 are as shown. to generate the same current. That is,

$$I_D(N3) = I_D(N4) = -I_D(P3) = -I_D(P4)$$

$$V_{TN} + \Delta V_N = V_{TN0} + \Delta V_N = -(V_{TP} + \Delta V_P) = -(V_{TP0} + \Delta V_P)$$

$$\Delta V_N = -\Delta V_P ; \text{ since } V_{TN0} = -V_{TP0}$$

Transistor MN3 and MP3 both have non-zero bulk to source voltage. Hence their threshold voltages increase. These values are computed as follows:

$$\begin{aligned}
V_{BS}(N3) &= V_B(N3) - V_S(N3) = V_{SS} - (V_{SS} + \Delta V_N) = -\Delta V_N \\
V_{TN} &= V_{TN0} + \gamma(\sqrt{\phi - V_{BS}} - \sqrt{\phi}) = V_{TN0} + \gamma(\sqrt{\phi + \Delta V_N} - \sqrt{\phi}) = 1 + 1(\sqrt{0.6 + 0.34} - \sqrt{0.6}) = 1.195 \\
V_{BS}(P3) &= V_B(P3) - V_S(P3) = V_{DD} - (V_{DD} + \Delta V_P) = -\Delta V_P \\
V_{TP} &= V_{TP0} - \gamma(\sqrt{\phi + V_{BS}} - \sqrt{\phi}) = V_{TP0} + \gamma(\sqrt{\phi - \Delta V_P} - \sqrt{\phi}) = -1 - 1(\sqrt{0.6 + 0.34} - \sqrt{0.6}) = -1.19
\end{aligned}$$

The value of the biasing voltage can now be calculated from the OTA circuit.

$$\begin{aligned}
V_{b4} &= V_{TN0} + \Delta V_N + V_{SS} = 1 + 0.34 + (-2.5) = -1.16 \\
V_{b3} &= V_{TN} + \Delta V_N + \Delta V_N + V_{SS} = 1.195 + 2(0.34) + (-2.5) = -0.625 \\
V_{b2} &= V_{DD} + \Delta V_P + V_{TP} + \Delta V_P = V_{DD} + V_{TP} + 2(\Delta V_P) = 2.5 - 1 + 2(-0.34) = 0.82 \\
V_{b1} &= V_{DD} + V_{TP0} + \Delta V_P = 2.5 - 1 - 0.34 = 1.16
\end{aligned}$$

The biasing circuit must determine the value of the divisor n to achieve the desired biasing voltages. V_{b4} and V_{b1} are satisfied by selecting the same transistor size as that of the OTA circuit. For V_{b3} and V_{b2} , the value of n must be determined to achieve the biasing voltages. The voltage on the biasing circuit side is determined and equated to the corresponding OTA bias voltage. This is illustrated as follows:

$$V_{b3} = V_{SS} + V_{TN0} + \Delta V_N + V_{TN} + \sqrt{n}\Delta V_N - (V_{TN} + \Delta V_N) = V_{TN0} + \sqrt{n}\Delta V_N + V_{SS}$$

Equating with corresponding equation in the OTA side, one obtains

$$\begin{aligned}
V_{TN0} + \sqrt{n}\Delta V_N + V_{SS} &= V_{TN} + 2(\Delta V_N) + V_{SS} \\
(\sqrt{n} - 2)\Delta V_N &= V_{TN} - V_{TN0} \\
n &= \left(\frac{V_{TN} - V_{TN0}}{\Delta V_N} + 2 \right)^2 = \left(\frac{1.195 - 1}{0.34} + 2 \right)^2 = 6.62 \approx 7
\end{aligned}$$

Similarly, V_{b2} on both sides are equated to obtain n, this value should be the same as that obtain for V_{b3} .

$$V_{b2} = V_{DD} + V_{TP0} + \Delta V_P + V_{TP} + \sqrt{n}\Delta V_P - (V_{TP} + \Delta V_P) = V_{DD} + V_{TP0} + \sqrt{n}\Delta V_P$$

Equating with corresponding equation in the OTA side, one obtains

$$\begin{aligned}
V_{DD} + V_{TP0} + \sqrt{n}\Delta V_P &= V_{DD} + V_{TP} + 2(\Delta V_P) \\
(\sqrt{n} - 2)\Delta V_P &= V_{TP} - V_{TP0} \\
n &= \left(\frac{V_{TP} - V_{TP0}}{\Delta V_P} + 2 \right)^2 = \left(\frac{-1.195 - (-1)}{-0.34} + 2 \right)^2 = 6.62 \approx 7
\end{aligned}$$

Figure 11 uses n=7 in the final implementation. The circuit using the subckt netlist of OTA in “wsotatf.cir” is simulated to show the internal node voltages. These voltages are shown below:

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
------	---------	------	---------	------	---------	------	---------

 

```

( 3) -1.1560 ( m1) 1.4886 ( m2) -1.0598 ( m3) 1.4454
( n1) 2.0839 ( n2) 2.0839 ( n3) -1.6585 ( n4) 1.1560
( n5) -2.1284 ( n6) -2.1284 ( n7) -2.1918 ( n8) 1.5124
( n9) 2.1589 ( in+) 0.0000 ( in-) 0.0000 ( vb1) 1.1771
( vb2) .7197 ( vb3) -.6744 ( vb4) -1.1587 ( vdd) 2.5000
( vss) -2.5000


```

The desired and actual biasing voltages are compared in the following table:

Biasing Voltage	Desired Value	Actual Value with n=7
Vb1	1.16	1.1771
Vb2	0.82	.7197
Vb3	-0.625	-0.6744
Vb4	-1.16	-1.1587



(a)

 

(b)

Actual 2 OTAs Circuit Implementation Netlist

```

*Filename = "univ2_a2.cir"
*Biquad 2nd order filter. fo=100K

```

```

Vin 1 0 DC 0V AC 1V
*LP
*Xs2flt 1 0 0 2 S2FLT
*HP
*Xs2flt 0 0 1 2 S2FLT
*BP
*Xs2flt 0 1 0 2 S2FLT
*BR
Xs2flt 1 0 1 2 S2FLT

```

```

.SUBCKT S2FLT v1 v2 v3 v0
.PARAM C=135.98pF
.PARAM Q=1.61803
Xotal v1 v0 n2 WSOTA
Xota2 n2 v0 v0 WSOTA

```

```

C1 n2 v2 {C/Q} IC=0V
C2 v0 v3 {Q*C} IC=0V
.ENDS

```

```

.SUBCKT WSOTA in+ in- out
* Power supplies
VDD vdd 0 DC 2.5V
VSS vss 0 DC -2.5V

```

* Wmin=Lmin=6 Lambda for linear analog circuit

```

.PARAM Wn=10.8U, Ln=3.6U
.PARAM Wp=32.4U, Lp=3.6U
.PARAM Wn7=3.6U, Ln7=8.4U
.PARAM Wp7=5.4U, Lp7=4.2U
.PARAM IB=10UA

```

* Biasing Circuit to generates vb1, vb2, vb3, vb4

```

MPB1 vb1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vb2 PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vb1 PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss {IB}

```

* Wide Swing OTA Implementation

```

MN1 n1 in+ n3 vss NMOS1 W={Wn} L={Ln}
MN2 n2 in- n3 vss NMOS1 W={Wn} L={Ln}
MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 out vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MN3 n3 vb3 n7 vss NMOS1 W={Wn} L={Ln}
MN4 n7 vb4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 out vb2 n2 vdd PMOS1 W={Wp} L={Lp}
MP1 n5 in+ n8 vdd PMOS1 W={Wp} L={Lp}
MP2 n6 in- n8 vdd PMOS1 W={Wp} L={Lp}
MP4 n9 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP3 n8 vb2 n9 vdd PMOS1 W={Wp} L={Lp}

```



```

.ENDS

.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9

* Analysis
.AC DEC 100 1Hz 100MegHz
.PROBE
.END

```

  

Actual 3 OTAs Circuit Implementation Netlist

```

*Filename = "univ2_a3.cir"
*Biquad 2nd order filter. fo=100K

Vin 1 0 DC 0V AC 1V
*LP
*Xs3flt 1 0 0 2 S3FLT
*HP
*Xs3flt 0 1 0 2 S3FLT
*BP
*Xs3flt 0 0 1 2 S3FLT
*BR
Xs3flt 1 1 0 2 S3FLT

.SUBCKT S3FLT v1 v2 v3 v0

```

```

.PARAM C=135.98pF
Xota1 v1 v0 n2 WSOTA
Xota2 n2 0 v0 WSOTA
Xota3 v3 v0 v0 WSOTA1
C1 n2 0 {C} IC=0V
C2 v0 v2 {C} IC=0V
.ENDS

.SUBCKT WSOTA in+ in- out
* Power supplies
VDD vdd 0 DC 2.5V
VSS vss 0 DC -2.5V

* Wmin=Lmin=6 Lambda for linear analog circuit
.PARAM Wn=10.8U, Ln=3.6U
.PARAM Wp=32.4U, Lp=3.6U
.PARAM Wn7=3.6U, Ln7=8.4U
.PARAM Wp7=5.4U, Lp7=4.2U
.PARAM IB=10UA

* Biasing Circuit to generates vb1, vb2, vb3, vb4
MPB1 vb1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vb2 PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vb1 PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss {IB}

* Wide Swing OTA Implementation
MN1 n1 in+ n3 vss NMOS1 W={Wn} L={Ln}
MN2 n2 in- n3 vss NMOS1 W={Wn} L={Ln}
MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 out vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MN3 n3 vb3 n7 vss NMOS1 W={Wn} L={Ln}
MN4 n7 vb4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 out vb2 n2 vdd PMOS1 W={Wp} L={Lp}
MP1 n5 in+ n8 vdd PMOS1 W={Wp} L={Lp}
MP2 n6 in- n8 vdd PMOS1 W={Wp} L={Lp}
MP4 n9 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP3 n8 vb2 n9 vdd PMOS1 W={Wp} L={Lp}
.ENDS

.SUBCKT WSOTA1 in+ in- out
* Power supplies
VDD vdd 0 DC 2.5V
VSS vss 0 DC -2.5V

* Wmin=Lmin=6 Lambda for linear analog circuit
.PARAM Wn=10.8U, Ln=3.6U
.PARAM Wp=32.4U, Lp=3.6U
.PARAM Wn7=3.6U, Ln7=8.4U
.PARAM Wp7=5.4U, Lp7=4.2U
.PARAM IB=3.8UA

```

```

* Biasing Circuit to generates vb1, vb2, vb3, vb4
MPB1 vb1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB2 m1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB3 vb2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MPB4 m3 m2 m1 vdd PMOS1 W={Wp} L={Lp}
MPB5 vss m2 vb2 vb2 PMOS1 W={Wp} L={Lp}
MPB0 m2 m2 vb1 vb1 PMOS1 W={Wp7} L={Lp7}
MNB0 m3 m3 vb4 vss NMOS1 W={Wn7} L={Ln7}
MNB1 vdd m3 vb3 vss NMOS1 W={Wn} L={Ln}
MNB2 vb4 vb4 vss vss NMOS1 W={Wn} L={Ln}
MNB3 vb3 vb4 vss vss NMOS1 W={Wn} L={Ln}
ISS m2 vss {IB}


* Wide Swing OTA Implementation
MN1 n1 in+ n3 vss NMOS1 W={Wn} L={Ln}
MN2 n2 in- n3 vss NMOS1 W={Wn} L={Ln}
MN5 n4 vb3 n5 vss NMOS1 W={Wn} L={Ln}
MN7 out vb3 n6 vss NMOS1 W={Wn} L={Ln}
MN6 n5 n4 vss vss NMOS1 W={Wn} L={Ln}
MN8 n6 n4 vss vss NMOS1 W={Wn} L={Ln}
MN3 n3 vb3 n7 vss NMOS1 W={Wn} L={Ln}
MN4 n7 vb4 vss vss NMOS1 W={Wn} L={Ln}
MP6 n1 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP8 n2 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP5 n4 vb2 n1 vdd PMOS1 W={Wp} L={Lp}
MP7 out vb2 n2 vdd PMOS1 W={Wp} L={Lp}
MP1 n5 in+ n8 vdd PMOS1 W={Wp} L={Lp}
MP2 n6 in- n8 vdd PMOS1 W={Wp} L={Lp}
MP4 n9 vb1 vdd vdd PMOS1 W={Wp} L={Lp}
MP3 n8 vb2 n9 vdd PMOS1 W={Wp} L={Lp}
.ENDS

.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9


* Analysis
.AC DEC 100 1Hz 100MegHz
.PROBE
.END

```

 
Frequency Response of Actual OTA Circuit Implementation



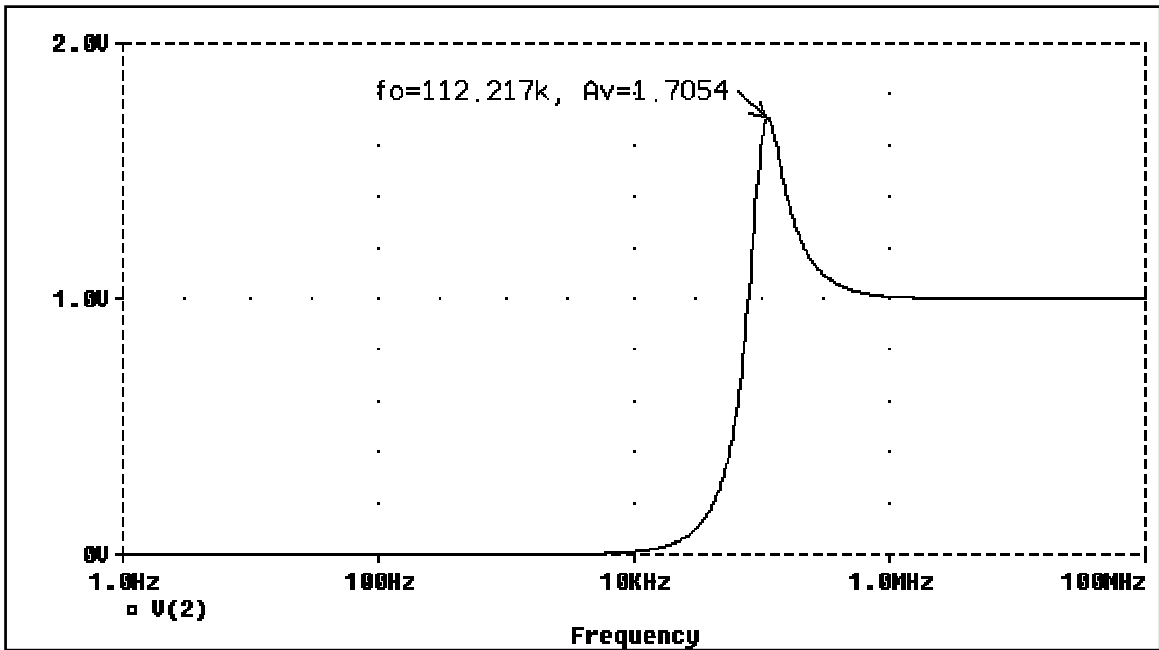
Implemented Second Order Lowpass Filter Response



 Implemented Second Order Highpass Filter Response



 Implemented Second Order Bandpass Response



Implemented Second Order Bandreject Response