

# Blocking and Desensitization in RF Amplifiers

Robert G. Meyer and Alvin K. Wong

**Abstract**—Blocking and desensitization in RF amplifiers is analyzed and related to second and third order intermodulation performance. Methods of predicting blocking behavior are described and used to improve the performance of an existing amplifier. Measurements are compared with theoretical predictions.

## I. INTRODUCTION

**P**REAMPLIFIERS in RF receivers are used to boost the incoming signal level prior to the frequency conversion process. This is important in order to prevent mixer noise from dominating the overall front-end noise performance. Important specifications of such RF amplifiers include noise figure, gain and third-order intermodulation intercept [1].

In typical applications, the RF receiver must tolerate large interfering signals emanating from users in adjacent channels, as well as from transmission sources which may be relatively far removed in frequency but whose large transmission power can cause significant interference problems. The influence of large interfering signals is manifested in several ways. One of these is third-order intermodulation in which two interfering signals at frequencies  $f_1$  and  $f_2$  (with  $f_1 \simeq f_2$  and both close to the desired signal) combine in the amplifier third-order nonlinearity to produce an intermodulation product at  $(2f_2 - f_1)$  which is again close to the desired signal. This intermodulation product is then processed by the receiver along with the desired signal. The resulting interference causes BER degradation in digital communication systems and audible or visible defects in analog communication systems. This is an example of desensitization in that the receiver sensitivity (ability to process very weak signals) is compromised by the presence of these intermodulation products. The relation between amplifier nonlinearity and intermodulation distortion is well-known and will not be considered further here.

Desensitization can also occur due to a single large interfering signal. This is called blocking and the interferer is called a blocker. In this paper the phenomenon of desensitization due to blocking is considered. The connection between blocking and amplifier nonlinearity is delineated and the results verified with experimental measurements.

## II. THEORETICAL ANALYSIS OF BLOCKING AND DESENSITIZATION IN AMPLIFIERS

The reduction in sensitivity in an amplifier caused by a large blocking signal can be attributed to two separate

Manuscript received October 18, 1994; revised February 3, 1995. This work supported by the U.S. Army Research Office under Grant DAAHO4-93-G-0200.

R. G. Meyer is with the Department of Electrical Engineering and Computer Sciences and the Electronics Research Laboratory, University of California, Berkeley, CA 94720 USA.

A. K. Wong is with Philips Semiconductors, Sunnyvale, CA 94086 USA.  
IEEE Log Number 9412009.

mechanisms. One of these is the gain compression caused by third-order nonlinearity in the circuit which occurs in the presence of large interfering signals, allowing existing noise sources in the amplifier (and in the mixer which usually follows it) to exert a larger influence, thus degrading the overall noise performance. The relationship between third-order nonlinearity and this gain compression can be analyzed assuming frequency independence of the nonlinearity [2] using a power series approach, or more generally for frequency dependent nonlinearities using Volterra series [3].

The second mechanism producing desensitization is caused by second-order nonlinearity in the circuit. In this case there is a mixing mechanism between (relatively) low-frequency noise sources in the amplifier and the interfering signal, which results in the low-frequency noise being up-converted to the desired signal frequency. This again degrades the circuit noise performance. Either one or both of these mechanisms may be significant in any given amplifier or receiver.

The phenomenon of gain compression caused by a large interfering signal acting on the amplifier third-order nonlinearity is well-known and the basic relations are summarized here for completeness. A power series representation is used for purposes of illustration and shows the same basic features as the more complex Volterra series approach.

Assume that the amplifier transfer function can be expanded in a power series as

$$V_o = a_1 V_i + a_2 V_i^2 + a_3 V_i^3 + \dots \quad (1)$$

where  $V_o$  is the output signal (bias removed),  $V_i$  is the input signal and coefficients  $a_1, a_2, a_3$  are frequency independent. Coefficient  $a_1$  is the small-signal gain. Consider a small wanted signal  $V_1 \cos \omega_1 t$  applied to the circuit together with a large interferer  $V_2 \cos \omega_2 t$ . Then

$$V_i = V_1 \cos \omega_1 t + V_2 \cos \omega_2 t. \quad (2)$$

Substituting (2) in (1) and collecting all terms at frequency  $\omega_1$  we have

$$V_o = a_1 V_1 \cos \omega_1 t + \frac{3}{2} a_3 V_1 V_2^2 \cos \omega_1 t + \dots \quad (3)$$

where the second term comes from the third-order nonlinearity. Thus the apparent gain of the circuit is

$$a'_1 = a_1 \left( 1 + \frac{3}{2} \frac{a_3}{a_1} V_2^2 \right). \quad (4)$$

A common method of characterizing this phenomenon is to specify the interfering signal level required to cause a  $-3$  dB gain compression. For this case we set

$$20 \log_{10} \left( 1 + \frac{3}{2} \frac{a_3}{a_1} V_2^2 \right) = -3$$

and assuming  $a_3$  and  $a_1$  have opposite signs we find

$$V_2 = 0.442 \sqrt{\frac{|a_1|}{|a_3|}}. \quad (5)$$

Thus the blocking level caused by third order effects is dependent on the ratio of coefficients  $a_1$  and  $a_3$ . This process is related to other third-order phenomena and a similar analysis to the above shows the 1 dB gain compression signal level (wanted signal only) is  $V_1 = 0.383 \sqrt{\frac{|a_1|}{|a_3|}}$ , or about 1 dB less than (5). Similarly the third-order intermodulation ( $IM_3$ ) intercept level can be calculated as  $V = 1.155 \sqrt{\frac{|a_1|}{|a_3|}}$ , or about 8 dB more than (5).

Desensitization can also occur from phenomena involving the second-order term in (1). Consider the small wanted signal  $V_1 \cos \omega_1 t$  applied to the amplifier together with a large interferer  $V_2 \cos \omega_2 t$  and a small interfering signal  $V_3 \cos \omega_3 t$ . Further assume that  $\omega_2$  is close to  $\omega_1$  and that  $\omega_3 \ll \omega_1$ . In practice, filters connected in front of the amplifier will usually ensure that practically no external signals at  $\omega_3$  (including external noise sources) are present at the amplifier active input node. However the amplifier itself has internal noise sources which act as unwanted signal inputs and are represented by  $V_3 \cos \omega_3 t$ . Thus

$$V_i = V_1 \cos \omega_1 t + V_2 \cos \omega_2 t + V_3 \cos \omega_3 t. \quad (6)$$

Substituting in (1), neglecting powers beyond the second and collecting the relevant terms we find

$$V_o = a_1 V_1 \cos \omega_1 t + a_2 V_2 V_3 \cos(\omega_2 \pm \omega_3)t + \dots \quad (7)$$

Since noise is present in the circuit at all frequencies,  $\omega_3$  can always be chosen so that the term generated at  $(\omega_2 \pm \omega_3)$  falls in the band occupied by the wanted signal at frequency  $\omega_1$ . This interference can thus be identified as a second-order intermodulation ( $IM_2$ ) effect with the amplifiers own internal noise acting as one input. The effect occurs for any values of  $\omega_2$  and  $\omega_3$  as long as  $(\omega_2 \pm \omega_3) \simeq \omega_1$ . However the worst case is usually found for  $\omega_2 \simeq \omega_1$  and  $\omega_3 \ll \omega_1$ . Excessive  $1/f$  noise levels in the circuit will also tend to make this phenomenon more pronounced.

From (7) the ratio of the interference to the amplitude of the wanted signal is  $\frac{|a_2|}{|a_1|} \frac{V_2 V_3}{V_1}$ . The second-order intermodulation intercept is  $V = \frac{|a_1|}{|a_2|}$ , and thus the desensitization produced by this blocking mechanism is directly related to the second-order intermodulation performance of the amplifier

### III. MEASUREMENT

The theory developed above was prompted by measurements on an existing RF amplifier described elsewhere [4]. A schematic is shown in Fig. 1. This is a 2-stage amplifier ( $Q_1$  and  $Q_2$ ) with overall dc feedback via  $Q_6$  used to stabilize the bias point. The feedback is decoupled in the kilohertz range by  $R_{14}$  and  $C_3$ . Bias currents are  $I_{C1} = 2.5$  mA,  $I_{B1} = 25$   $\mu$ A, and  $I_{C2} = 5.5$  mA with a supply voltage of 5 V. Peak process  $f_T$  is 10 GHz with base resistance for the large area input device  $Q_1$  of 11  $\Omega$ . The input blocking signal power level

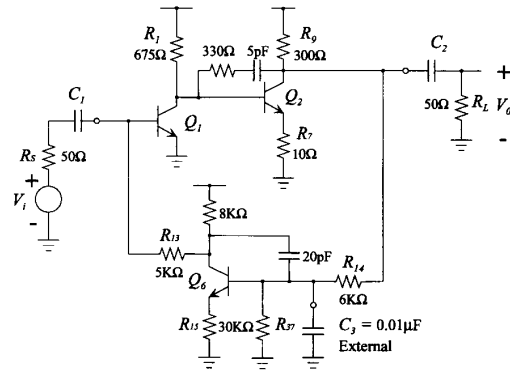


Fig. 1. RF amplifier schematic.

required to cause a  $-3$  dB gain compression in the amplifier at 950 MHz was measured as  $-20$  dBm at the input. The 1 dB gain compression level was also about  $-20$  dBm and the third-order intercept was  $-10$  dBm. These results agree closely with the theoretical predictions above for third-order blocking.

Blocking due to second-order effects was also observed in that large interfering signals at 950 MHz (offset by 3 MHz from the desired channel) representing adjacent channels caused significant increases in the background noise of the amplifier at 947 MHz. In order to predict these effects analytically, information is needed on both the noise generators of the amplifier at 3 MHz and the value of  $IM_2$  for  $f_2 = 950$  MHz and  $f_3 = 3$  MHz. Equivalent input noise generators for the amplifier are conveniently generated using SPICE. Noise from all generators in the circuit is first calculated at  $V_o$  and then referred back to the input as a current generator across the base-emitter of  $Q_1$ . At 3 MHz this gave an equivalent input noise current spectral density of 25.4 pA/ $\sqrt{\text{Hz}}$ .

Levels of  $IM_2$  in the circuit can be determined from simulation or from measurements. Since the measurements are quite straightforward whereas the simulation is dependent on the fine detail and accuracy of the large-signal device models, the  $IM_2$  data was generated by measurement in the circuit shown in Fig. 2. A small signal  $V_{i2}$  at 3 MHz representing circuit noise is injected into the input via a 2 K $\Omega$  resistor. A large blocking signal  $V_{i1}$  at 950 MHz is injected at the input and the  $IM_2$  product at  $V_o$  measured on a spectrum analyzer. For a power level of  $-54$  dBm delivered to the circuit from  $V_{i2}$  and  $-23$  dBm (the blocking level specification of interest) the measured  $IM_2$  product at  $V_o$  was  $-60.1$  dBm. The  $IM_2$  product varied approximately 1 dB per dB variation in  $V_{i1}$  or  $V_{i2}$ , as predicted by theory. The power level of  $-54$  dBm at 3 MHz represents 0.446 mV rms delivered to 50  $\Omega$ . Taking a Norton equivalent at the amplifier input through the 2 K $\Omega$  resistor gives an input current  $I_i = 0.446$  mV/2 K $\Omega = 0.223$   $\mu$ A rms. This gave a measured output from the amplifier at 947 MHz of  $-60$  dBm, which is 223  $\mu$ V rms. Thus the transfer function of the amplifier from noise current input at 3 MHz to voltage out at 947 MHz in the presence of a  $-23$  dBm blocker at 950 MHz is

$$\frac{V_o}{I_i} = \frac{223 \times 10^{-6}}{0.223 \times 10^{-6}} = 1K\Omega. \quad (8)$$

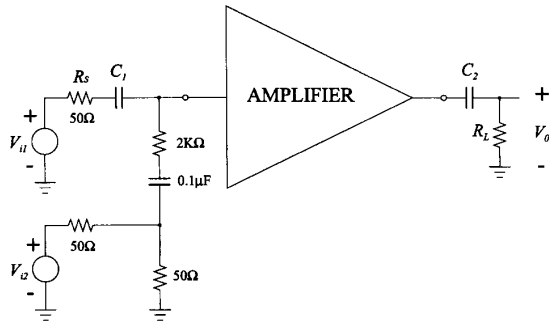


Fig. 2. Test circuit for  $IM_2$  measurements.

Thus the SPICE simulated equivalent input noise current density of  $25.4 \text{ pA}/\sqrt{\text{Hz}}$  at 3 MHz should give an output noise voltage density of  $25.4 \text{ nV}/\sqrt{\text{Hz}}$ .

The desensitization caused by second-order blocking can now be calculated. First, the noise floor of the amplifier with no blocker can be calculated from the measured gain (15.5 dB) and noise figure (2.4 dB) at 947 MHz. This gives an output noise 17.9 dB above the input noise in  $50 \Omega$  (which is  $\sqrt{kTR} = 0.445 \text{ nV}/\sqrt{\text{Hz}}$ ). Thus the output noise from the amplifier at 947 MHz is  $3.5 \text{ nV}/\sqrt{\text{Hz}}$  or  $-156 \text{ dBm}/\sqrt{\text{Hz}}$  with no blocker present. In the presence of the 950 MHz blocker at  $-23 \text{ dBm}$  the output noise is increased by the  $25.4 \text{ nV}/\sqrt{\text{Hz}}$  calculated above. This is added to the amplifier output noise which is itself compressed somewhat by the third order blocking effect to  $3 \text{ nV}/\sqrt{\text{Hz}}$ . The rms combination of these two gives a predicted output noise of  $25.6 \text{ nV}/\sqrt{\text{Hz}}$  which is  $-138.8 \text{ dBm}/\sqrt{\text{Hz}}$ . The measured output noise under these conditions was  $-139.1 \text{ dBm}/\sqrt{\text{Hz}}$ , a very close agreement. Note that the noise floor has risen 17 dB from the value with no blocker present.

The theoretical understanding of the blocking phenomenon described above allows investigation of methods of improving blocking performance. The equivalent input noise of the amplifier is not easily decreased but the  $IM_2$  performance can be enhanced in several ways. One of these is to increase the

bias current in  $Q_2$  by adding a  $1 \text{ k}\Omega$  pull-up resistor from the collector of  $Q_2$  to  $V_{CC}$ . This increases the output stage bias current by several mA and improves the large signal handling capability of the amplifier. The measured  $IM_2$  product at 947 MHz was then reduced by 10 dB to  $-70.0 \text{ dBm}$  for  $V_{i1}$  of  $-23 \text{ dBm}$  and  $V_{i2}$  of  $-54 \text{ dBm}$  in the test described previously. A similar calculation to that described previously predicts that the noise output of the amplifier is increased by  $8.0 \text{ nV}/\sqrt{\text{Hz}}$  due to second-order blocking, and that the total output noise should be  $-148.4 \text{ dBm}/\sqrt{\text{Hz}}$ . The measured noise was  $-148.1 \text{ dBm}/\sqrt{\text{Hz}}$  with this modification.

The  $IM_2$  performance can be further improved by reducing the low-frequency gain of the amplifier. This reduces the signal level in the circuit at frequency  $f_3$  and can be accomplished by adding a bypassed resistor in series with  $R_7$  in Fig. 1. A parallel  $RC$  network consisting of  $10 \Omega$  in parallel with  $390 \text{ pF}$  added in this way further reduced the measured  $IM_2$  product in the circuit at 947 MHz to  $-78 \text{ dBm}$ . The added noise output of the amplifier caused by second-order blocking is then predicted to be  $3.2 \text{ nV}/\sqrt{\text{Hz}}$  and the total output noise  $-153.4 \text{ dBm}/\sqrt{\text{Hz}}$ . The measured noise was  $-152.1 \text{ dBm}/\sqrt{\text{Hz}}$  with these modifications.

#### IV. CONCLUSIONS

Blocking and desensitization in RF amplifiers can be predicted from second and third order intermodulation performance and amplifier noise parameters. Good agreement is obtained between measured and predicted blocking performance in a practical amplifier, and circuit modifications to improve performance are described.

#### REFERENCES

- [1] R. S. Carson, *Radio Communications Concepts: Analog*. New York: Wiley, 1990.
- [2] K. A. Simons, "The decibel relationship between amplifier distortion products," *Proc. IEEE*, vol. 58, pp. 1071-1086, July 1970.
- [3] D. A. Weiner and J. F. Spina, *Sinusoidal Analysis and Modeling of Weakly Nonlinear Circuits*. New York: Van Nostrand Reinhold, 1980.
- [4] R. G. Meyer and W. D. Mack, "A 1-GHz BiCMOS RF front-end IC," *IEEE J. Solid-State Circuits*, vol. 29, pp. 350-355, Mar. 1994.